

Unit 04-

Op - Amp


(Operational Amplifiers)

High gain, direct coupled, differential amplifier and can perform multiple operations [mathematical]. Coupling / biasing capacitors - blocks. DC and couples AC disadvantage - \rightarrow No DC op is possible, amplification of DC is not possible as it is blocked.


Differential amplifier

Consider the difference b/w P/P signals and blocks all common-mode signals like noise etc.

Block diagram

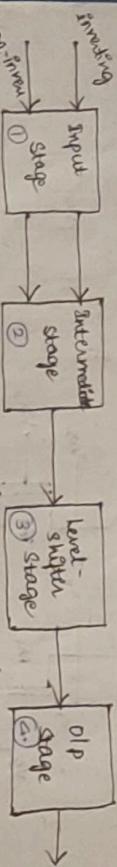

[provides cascading) overall high gain]

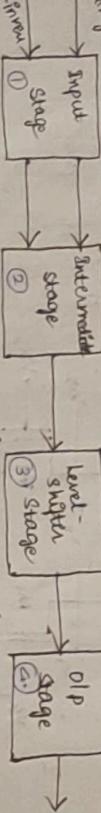

should always reflect common-mode input impedance - where should be present output diff amplifier. Introduces high gain.

- ① we find stage 1 should always reflect common-mode input impedance - where should be present output diff amplifier. Introduces high gain.
- ② we cascaded stage 1 and stage 2. Also introduces high gain as it is differential amplifier.
- ③ we accumulation of DC leads to operating point shift. And due to which signal will be lost to clipping.

[there might be offset] [in no. 1 and 2 of op-amp see for offset adjustment]


[in no. 1 null the DC] [class B power amplifier is used.]

(4) Power amplifier/OP stage: Class B power amplifier is used. Current is also amplified and small resistance is used resistors - one more preferred due to device stability.

[OP is used] [low collector current gives low op impedance]

[low collector current gives low op resistance]

Symbol of op-amp:

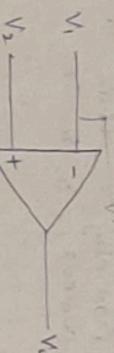

No-OP V_1 - inverting op. V_2 - non-inverting op.

Op. Gain ($V_2 - V_1$) [non-inverting - inverting]

Op. Gain differential voltage

Parameters/Characteristics of op-amp

Ideal

R_{in} ∞ O Low impedance low for voltage amplifier

R_{out} ∞ BW ∞

A_v ∞ $CMRR$ ∞

$slew rate$ ∞ $\frac{dV_o}{dt} \rightarrow$ now fast the op-amp responds [OP] with change in op. frequency applications.

Applications :- $\frac{dV_o}{dt}$ low fast the op-amp responds [OP] with change in op. frequency applications.

Open loop :- no feedback resistance is present the $\frac{dV_o}{dt}$ closed loop :- feedback resistance is present \rightarrow $-ve A_B$

Other op-amp parameters:

Op. offset voltage: When $OP = 0$ [not applied] op-amp should be zero.


Op. offset current: The current applied in order to make $V_{op} = 0$.

Op. offset voltage: The small voltage applied when OP is zero.

Op. offset voltage: The small voltage is zero [mostly due to level shifter].

$\text{Op-amp bias current}$ - Ideally, input current is zero.

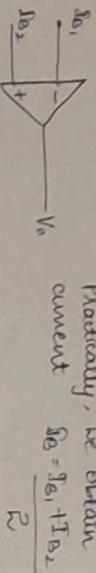Practically, we obtain a small bias current $I_B = I_{B1} + I_{B2}$



Output offset voltage is due to $\text{Op-amp offset voltage}$ and bias current .

$\rightarrow \text{Power supply Rejection Ratio: } [\text{Ideal} = 0]$

$\frac{\Delta V_{os}}{\Delta V_{cc}}$ is change in output offset voltage due to change in supply - the ratio is PSRR.

Diff: the change in values of parameters with time and change in temperature.

Op-amp ESR

negative feedback: when feedback is in phase with the op-amp ESR

positive feedback: when feedback is out of phase with the op-amp ESR

not supporting it.

Open loop application:


\rightarrow Inverting \leftarrow -ve ref.

\rightarrow Non-inverting \leftarrow the ref.

\rightarrow Zener-crossing detector:

\rightarrow Schmitt trigger

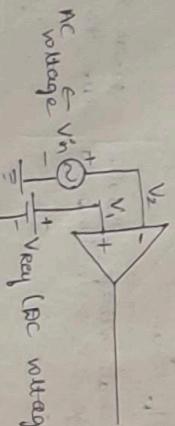
(i) Inverting comparator: [case i: with two references] Input is given at the inverting terminal



$$V_0 = A_{ad}(V_1 - V_2) \quad [\text{non-inverting - inverting}]$$


$$V_1 = V_{ref} \quad V_2 = V_{in}$$

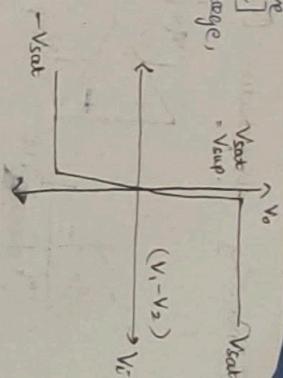Where $V_{ref} > V_{in}$, gain is positive and op-amp will go to saturation [the sat]. It is V_{sat} is supply voltage, but difference is due to device.




Applying any wave can be converted into square wave. and clipping point is V_{sat} .

V_{sat}

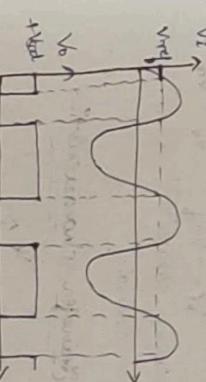

Transfer characteristic

V_{sat} - clipping points

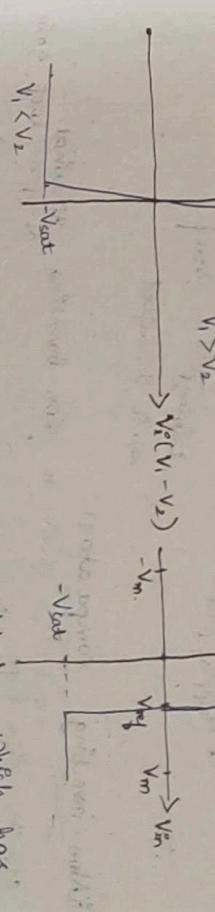

V_{sat}


V_{sat}

V_{sat}

V_{sat}

because gain is added which has a cap. of V_{sat} , hence op-amp is $\pm V_{sat}$ irrespective of op-amp. [ideally, assuming gain is ∞)

⑥ Inverting comparator (-ve ref)

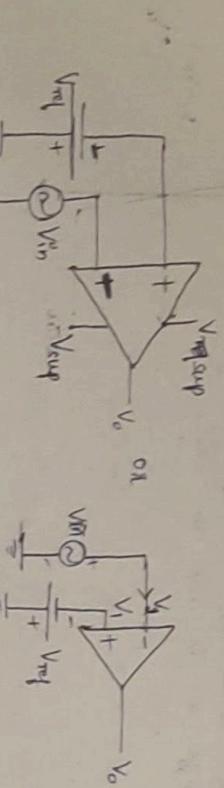

$$V_o = A_{OL}(V_1 - V_2)$$



$$V_1 = -V_{ref}$$

$$V_2 = V_{in}$$

$V_{in} < V_{ref}$, then op is positive saturation.


$V_{in} > V_{ref}$, then op is -ve saturation.

Transfer characteristics

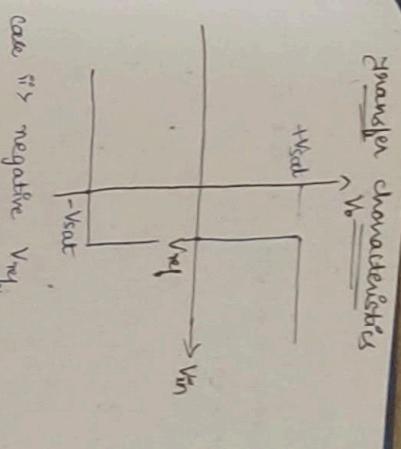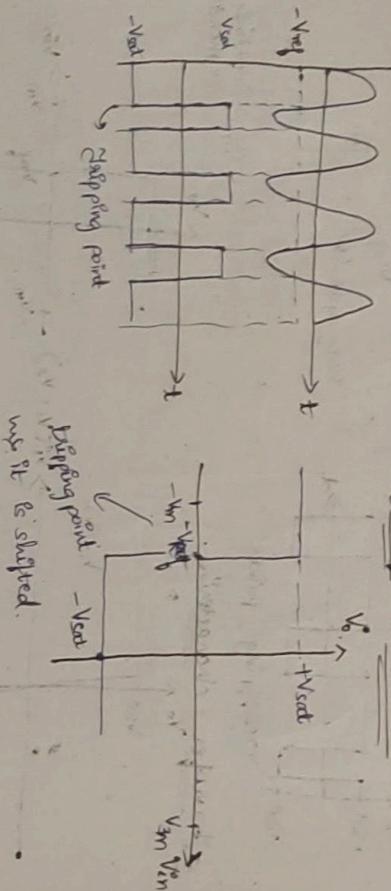

⑦ Non-inverting comparator :-

case i) positive V_{ref}

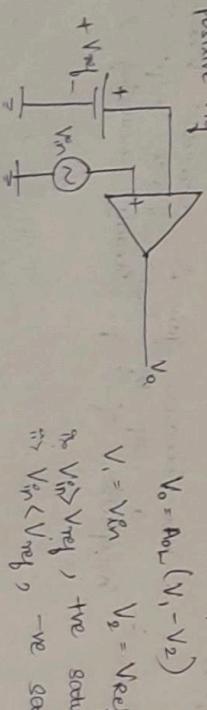

case ii) given to non-inverting terminal open loop gain.


$$V_o = A_{OL}(V_1 - V_2)$$

$$V_1 = V_{in}$$

$$V_2 = V_{ref}$$


$V_{in} > V_{ref}$, the saturation

$V_{in} < V_{ref}$, -ve saturation.

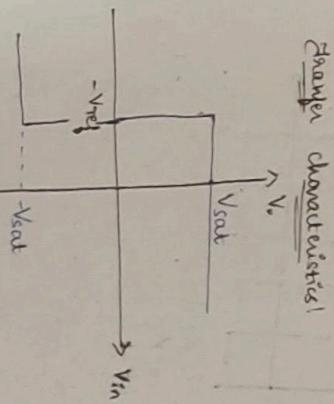


(iii) Zero Crossing Detector



if V_P is given to inverting terminal.

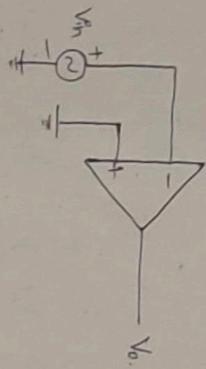

Transfer characteristics

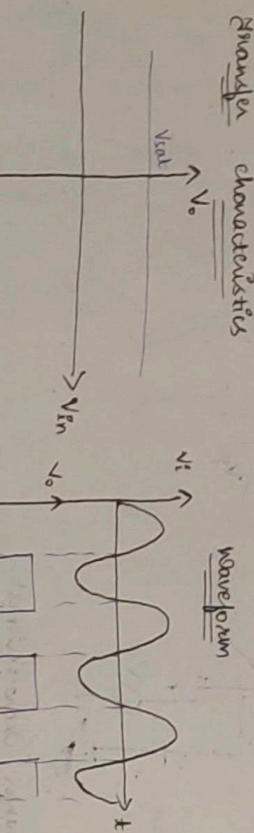

Waveform

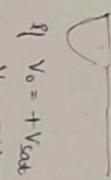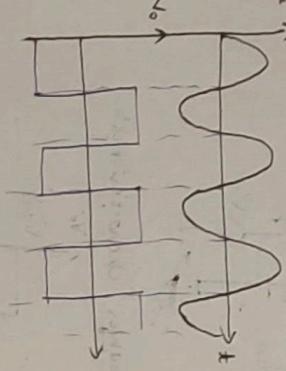

$$V_o = +V_{sat}$$

$$V_{rel} = V_{TP}$$

$$V_{rel} = V_{TP} = \frac{+V_{sat} \cdot R_2}{R_1 + R_2}$$


$$V_{TP_2} = \frac{V_{rel} \cdot R_1}{R_1 + R_2}$$

$$\therefore V_{TP} = +V_{sat} \cdot \frac{R_2}{R_1 + R_2} + \frac{V_{rel} \cdot R_1}{R_1 + R_2}$$

$$V_{rel} = V_{sat}$$

$$V_{rel} = V_{TP} = -V_{sat} \cdot \frac{R_2}{R_1 + R_2} + \frac{V_{rel} \cdot R_1}{R_1 + R_2}$$

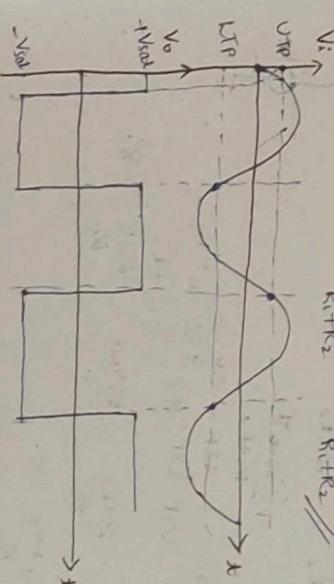
$V_{TP} = L_{TP}$
duty cycle is
 $T_{off} = T_{on}$



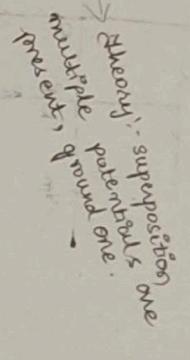
(iv) Schmitt trigger based on inverting comparator

[inverting voltage at non-inverting terminal is zero if there is no negative feedback, gain is very large.]

if there is no negative feedback, gain is very large.
output can either be positive saturation.



Biasing circuit

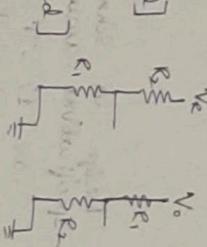


Application:

* Window level detector (V_{TP} and V_{LP}).
* Analog signal is converted into square wave.
* May signal characteristics [V_{TP} - V_{LP} characteristics]

Transfer characteristics [V_o]

Characteristics

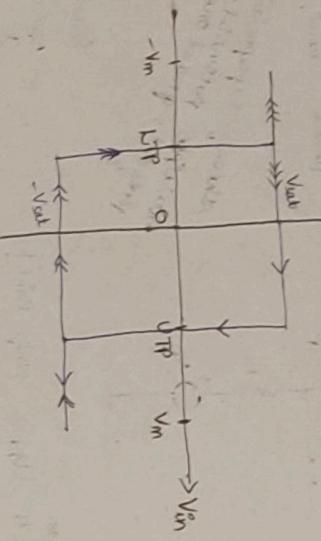

Design a Schmitt trigger for the following specifications, assume $+V_{sat} = \pm 15V$.

case 1: $V_{TP} = +5V$ $V_{LP} = -5V$

case 2: $V_{TP} = +4V$ $V_{LP} = -6V$

case 3: $V_{TP} = +8V$ $V_{LP} = -4V$

case 4: $V_{TP} = +7V$ $V_{LP} = -7V$

case 5: $V_{TP} = -1V$

$$\text{SOLN: } V_{TP} = \frac{-V_{sat}R_2}{R_1+R_2} + \frac{V_{in}R_1}{R_1+R_2}$$


$$V_{LP} = \frac{V_{in}R_1}{R_1+R_2} + \frac{(-V_{sat})R_2}{R_1+R_2}$$

case 5: $V_{TP} = 3V$ $V_{LP} = -3V$

step 1: $V_{TP} - V_{LP} = 6 = 2 \times V_{sat} \times R_2$

$$\frac{R_1+R_2}{R_2} = \frac{2 \times V_{sat}}{6} = \frac{2 \times 15}{6} = 5$$

$$\frac{R_1+R_2}{R_2} > 5$$

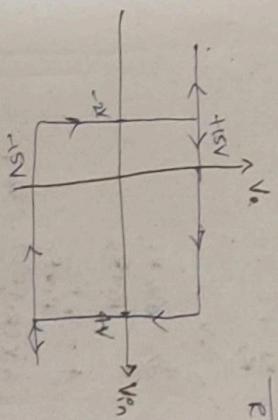

$$\frac{R_1}{R_2} + 1 = 5$$

$$\frac{R_1}{R_2} = 4$$

$$\text{for } R_2 = 10k\Omega$$

$$\therefore R_1 = 40k\Omega$$

$$\text{Step 2: } V_{TP} = 5V \quad V_{LP} = -5V$$

$$O = \frac{2VR_1}{R_1+R_2} \quad \text{As } R_1, R_2 \text{ cannot be } 3000.$$

$$\boxed{VR = 0}$$

$$\text{Case 2: } V_{TP} = 4V \quad V_{LP} = -6V$$

$$\text{Step 3: } V_{TP} - V_{LP} = 6 = \frac{2V_{sat}R_2}{R_1+R_2}$$

$$\frac{R_1+R_2}{R_2} = \frac{2V_{sat}}{6} = \frac{2 \times 15}{6} = 5$$

$$\frac{R_1}{R_2} + 1 = 5$$

$$\frac{R_1}{R_2} = 4$$

$$\text{Assume } R_2 = 10k\Omega$$

$$\therefore R_1 = 40k\Omega$$


All window size is same, resistance ratio is same
(independent)

$$\text{Step 4: } V_{TP} + V_{LP} = 6 = \frac{2VR_1}{R_1+R_2}$$

$$\frac{R_1}{R_2} + 1 = 6$$

$$\frac{V_{in}R_1}{R_1+R_2} = 1$$
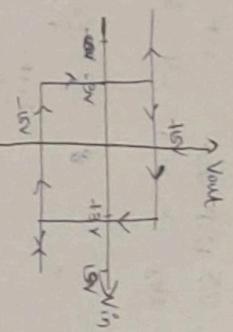
$$V_{in} = \frac{R_1+R_2}{R_1} = \frac{50k\Omega}{40k\Omega} = \frac{5}{4} = 1.25V$$



$$V_C = \frac{A \times (R_2)}{R_1 + R_2} \quad V_C = 4.5V$$

case 1) $\Rightarrow UTP = 2V$ LTP = -4V
 step 2) $\Rightarrow UTP - LTP = 6V = \frac{\Delta V_{out} R_2}{R_1 + R_2}$

$$3 = \frac{V_{out} R_2}{R_1 + R_2}$$

$$\frac{R_1 + R_2}{R_2} > \frac{V_{out}}{3} = \frac{5}{3} \text{ or } \approx 1.67V$$

$$\frac{R_1 + R_2}{R_2} > 5 \quad \text{Assume } R_2 = 10k\Omega \quad R_1 = 40k\Omega$$

$$\frac{R_1}{R_2} = 4V$$

Step ⑥) $UTP + LTP = -AV = \frac{\Delta V_{out} R_1}{R_1 + R_2}$

$$-I = \frac{V_C R_1}{R_1 + R_2}$$

$$V_C = -\frac{(R_1 + R_2)}{R_1} = -\frac{50k\Omega}{40k\Omega} = -1.25V$$

case 3) $\Rightarrow UTP = 1V$ LTP = 1V
 step 4) $\Rightarrow UTP - LTP = 2V = \frac{\Delta V_{out} R_2}{R_1 + R_2}$

$$3 = \frac{V_{out} R_2}{R_1 + R_2}$$

$$R_2 = 10k\Omega$$

$$\frac{V_{out}}{3} = \frac{R_1 + R_2}{R_1 \cdot 10k\Omega}$$

$$\frac{5}{3} = \frac{R_1 + 10k\Omega}{R_1 + 10k\Omega}$$

$$\frac{5}{3} = \frac{1}{1 + \frac{10k\Omega}{R_1}}$$

$$\frac{5}{3} = \frac{1}{1 + \frac{10k\Omega}{R_1}}$$

$$\text{step 5) } UTP + LTP = -AV = \frac{\Delta V_{out} R_1}{R_1 + R_2}$$

$$4 = \frac{V_C R_1}{R_1 + R_2}$$

$$4 \times \frac{R_1}{R_1 + R_2} = V_C$$

case 4) $\Rightarrow UTP = -1V$ LTP = -7V
 step 5) $\Rightarrow UTP - LTP = 6V = \frac{\Delta V_{out} R_2}{R_1 + R_2}$

$$3 = \frac{V_{out} R_2}{R_1 + R_2}$$

$$\frac{V_{out}}{3} = \frac{R_1 + R_2}{R_2} \Rightarrow \frac{5}{3} = \frac{R_1}{R_2} + 1$$

$$R_2 = 10k\Omega \quad \text{Assume } R_1 = 40k\Omega \quad R_2 = 40k\Omega$$

$$\frac{R_1 + R_2}{R_2} = \frac{10}{3}$$


Step 6) $UTP + LTP = -AV = \frac{\Delta V_{out} R_1}{R_1 + R_2}$
 $-4 = \frac{V_C R_1}{R_1 + R_2} \Rightarrow -4 = \frac{V_C (40k\Omega)}{50k\Omega}$

$$\Rightarrow -\frac{4 \times 50k\Omega}{40k\Omega} = V_C$$

$$V_C = -5V$$

$$\therefore 2-3$$

Design

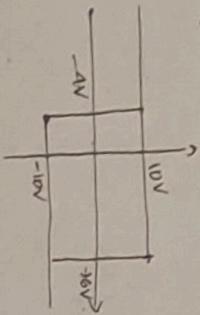

$$V_{TP} = 6V$$

$$\text{Step 1: } V_{TP} - L_{TP} = \frac{5}{4}V = \frac{\Delta V_{sat}}{R_1 + R_2} R_2$$

$$S = V_{sat} R_2$$

$$\frac{R_1 + R_2}{R_1} = \frac{10^2}{8}$$

$$R_1 = R_2$$

$$\frac{R_1}{R_2} + 1 = 2$$

$$S = V_{sat} R_2$$

$$R_1 = R_2$$

$$\text{Step 2: } V_{TP} + L_{TP} = \frac{1}{2}V = \frac{\Delta V_{sat} R_1}{R_1 + R_2}$$


$$V_o = (A_{OL}) V_{dA}$$

$$V_{dA}(\max) = \frac{V_{o(\max)}}{A_{OL}} = \frac{15}{10^5} = 150 \mu V / 0.015mV$$


Not much voltage greater than 0.15mV, the op-amp saturates and again is not observed according to $V_o = A_{OL}(V_{dA})$

Negative feedback
A part of op-amp is fed back via "IP" which is out of phase, hence termed as -ve feedback.

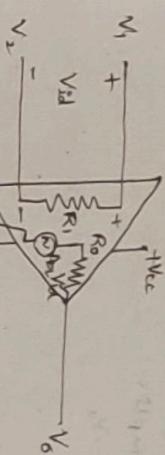Equivalent circuit of op-amp [closed loop]



Characteristics

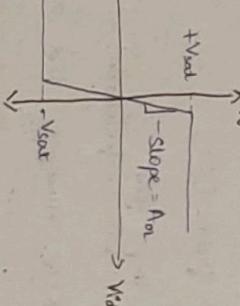


$$V_o = V_{sat} > \pm 15V$$

$$A_{OL} = 10^5$$

$$V_{dA} = ?$$

$$V_{dA}(\max) = \frac{V_{o(\max)}}{A_{OL}} = \frac{15}{10^5} = 150 \mu V / 0.015mV$$

Negative feedback

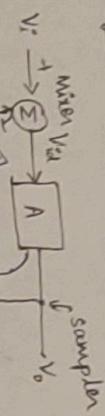

A - open loop gain - A_{OL}

$$\text{where } A_{OL} = A = \frac{V_o}{V_{id}}$$

$$\therefore V_1 = V_i - V_f$$

where $\beta = \text{feedback factor} (<1)$

$$A_F = \frac{V_o}{V_i}$$

(Gain with feedback)


$$A_F = \frac{V_o}{V_i} = \frac{V_o}{V_{id} + V_f} \quad \text{divide numerator and denominator by } V_{id}.$$

$$A_F = \frac{V_o}{V_{id}} \cdot \frac{V_{id}}{V_{id} + V_f}$$

$$A_F = \frac{V_o / V_{id}}{1 + \frac{V_f}{V_{id}}} = \frac{A_{OL}}{1 + A_{OL}\beta}$$


$A_{OL} = \frac{V_o / V_{id}}{1 + \frac{V_f}{V_{id}}} = \frac{A_{OL}}{1 + A_{OL}\beta}$
[Gain is reduced]

No loop gain
characteristics

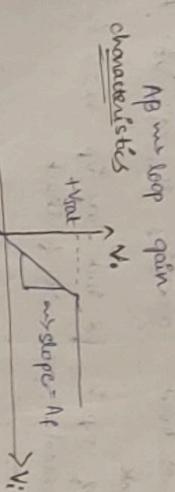

Closed loop application
non-inverting amplifier \rightarrow voltage follower
summing difference amplifier
no differentiation

Virtual ground

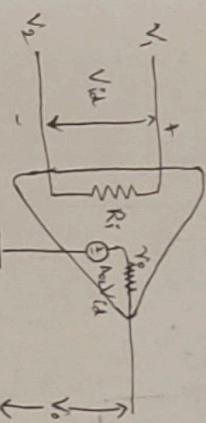

$$V_o = A_{OL}V_{id} = A_{OL}(V_1 - V_2) \quad \text{or } A_{OL} = \frac{V_o}{V_1 - V_2}$$


$$V_1 - V_2 = 0$$

as $V_1 = V_2$ \Rightarrow this condition holds good when one terminal is physically grounded and other

terminal becomes virtually grounded.
Since, $R_1 = 0$ [input current $I_1 = I_2 = 0$]


R_1 , current is zero.

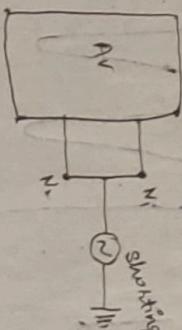through the resistor R_1 , current is zero.
two nodes N_1 and N_2 are shorted, voltage is zero,
no current may not exist and in open circuit
current may not exist and may be non-zero.
 V_o is zero and voltage and current are non-zero.
 V_{id} is zero and current are non-zero.
virtual ground, voltage and current are zero.



Non-inverting amplifier

(5) Ideal case by virtual ground

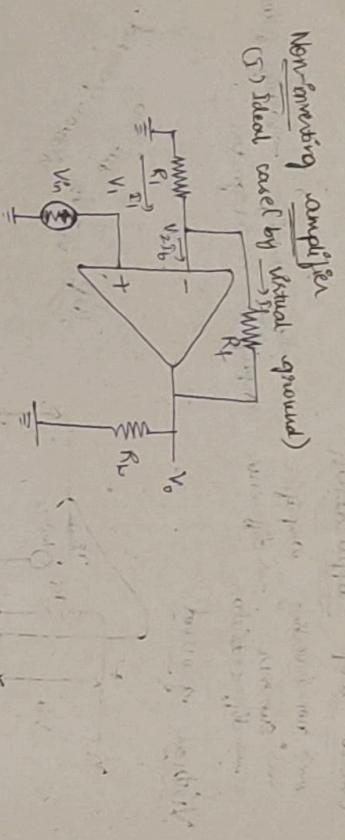

KCL at node 2

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \dots + \frac{V_n}{R_n} = -\frac{V_o}{R_f}$$

$$V_o = -\left(\frac{R_f}{R_1}V_1 + \frac{R_f}{R_2}V_2 + \frac{R_f}{R_3}V_3 + \dots + \frac{R_f}{R_n}V_n\right)$$

*** summing(inverting) & a scaling amplifiers.**


① In eqn ①, if we consider $R_1 = R_2 = \dots = R_n = R$

$$Then eqn \Rightarrow V_o = -\frac{R_f}{R}(V_1 + V_2 + V_3 + \dots + V_n)$$

② If in eqn ①, if we consider $R_f = R_1 = R_2 = \dots = R_n = R$

$$Then eqn \Rightarrow V_o = -(V_1 + V_2 + V_3 + \dots + V_n)$$

Summer (Inverting)

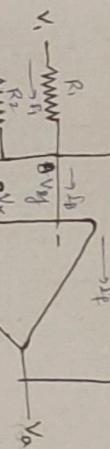

KCL at node 2

$$V_1 + V_2 + V_3 + \dots + V_n = \frac{V_o}{R_f} + \frac{V_o}{R_L}$$

$$V_o = 0 \text{ (by virtual ground)} \quad [R_f = \infty]$$

$$V_o = \frac{V_1 - V_2 + V_3 - V_4 + \dots + V_{n-1} - V_n}{R_2 - R_1}$$

But $V_2 = V_4 = 0$ [virtual ground]

$$\frac{V_1}{R_1} + \frac{V_3}{R_3} + \dots + \frac{V_n}{R_n} = -\frac{V_o}{R_f}$$

$$V_o = -\left(\frac{R_f}{R_1}V_1 + \frac{R_f}{R_3}V_3 + \dots + \frac{R_f}{R_n}V_n\right)$$

*** summing(inverting) & a scaling amplifiers.**


① In eqn ①, if we consider $R_1 = R_3 = \dots = R_n = R$

$$Then eqn \Rightarrow V_o = -\frac{R_f}{R}(V_1 + V_3 + V_5 + \dots + V_n)$$

② If in eqn ①, if we consider $R_f = R_1 = R_3 = \dots = R_n = R$

$$Then eqn \Rightarrow V_o = -(V_1 + V_3 + V_5 + \dots + V_n)$$


Differential amplifier (subtractor)

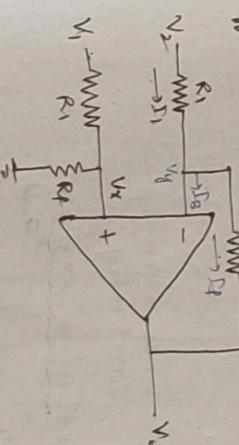



$$A_v = 1 + \frac{R_f}{R_1}$$

V_o can be obtained by applying superposition theorem

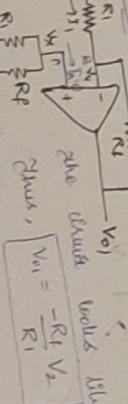$T \cdot \underline{V_1}$ alone
the output voltage is an inverting amplifier



$\underline{V_2}$ alone

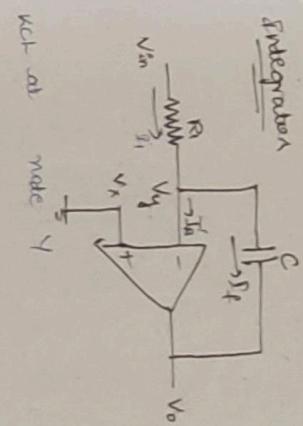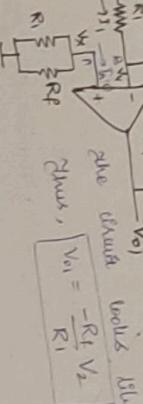

$$\frac{V_i - V_y}{R_1} = C \frac{d(V_y - V_o)}{dt}$$

$$V_y = V_x = 0 \text{ [virtual ground]}$$

$$\frac{V_i}{R_1} = -C \frac{dV_o}{dt} \quad \rightarrow \quad \frac{V_i}{R_1} = -C \frac{dV_o}{dt}$$

$$dV_o = -\frac{1}{RC} dt$$

$$\text{Integrate the eqn}$$

$$V_o(t) = -\frac{1}{RC} \int V_i dt$$

Note: $RC \gg T$ will result acts as an integrator.

Using super-position theorem

$$V_o = V_{o1} + V_{o2}$$

$$= -\frac{R_2}{R_1} V_2 + \frac{R_4}{R_1} V_1$$

$$V_o = \frac{R_4}{R_1} (V_1 - V_2)$$


$$V_1 \text{ non-inverting}$$

$$V_2 \text{ inverting}$$


$$V_o = V_1 - V_2 \text{ subtraction}$$

$$R_1 = R_2 = R$$

$$V_o = V_1 - V_2$$

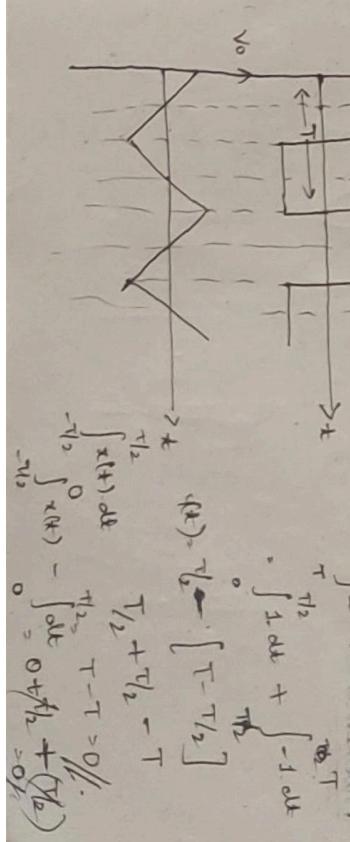

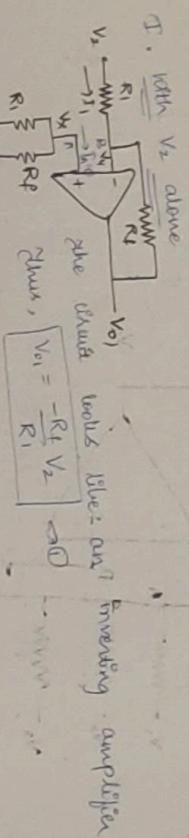
V_o can be obtained by applying superposition theorem.



$\therefore V_1 = -\frac{R_4}{R_1} V_2 \quad \text{---(1)}$

$$\text{Thus, } V_1 = \frac{-R_4}{R_1} V_2$$

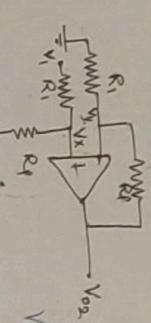$\therefore \text{With } V_1 \text{ alone}$



The circuit looks like a non-inverting amplifier.

$$V_{11} = \left(1 + \frac{R_4}{R_1}\right) V_x \quad \text{---(2)}$$

where $V_x = \frac{R_4}{R_1 + R_4} V_1$ [voltage division rule]

$$\text{---(3)}$$

$$= \left(\frac{R_4 + R_1}{R_1}\right) \left(\frac{R_4}{R_1 + R_4}\right) V_1$$

$$V_{12} = \frac{R_4}{R_1} V_1 \quad \text{---(4)}$$

Using super-position theorem


$$V_o = V_{11} + V_{12}$$

$$= -\frac{R_4}{R_1} V_2 + R_4 V_1$$

non-inverting
V₁₁, non-inverting

$$V_o = \frac{R_4}{R_1} (V_1 - V_2)$$

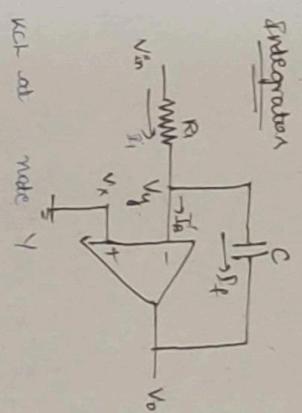$\therefore V_o = V_1 - V_2$ w/o substitution
difference amplifier



KCL at node Y

$$I_1 = I_2 + I_3$$

$$I_2 = 0 \quad [\text{by common ground}]$$

$$\frac{V_i - V_y}{R_1} = C \frac{dV_y}{dt}$$

$$V_y = V_x = 0 \quad [\text{virtual ground}]$$

$$\frac{V_i}{R_1} = -C \frac{dV_o}{dt} \quad \rightarrow \quad \frac{V_i}{R_1} = -C \frac{dV_o}{dt}$$

$$dV_o = -\frac{1}{RC} V_i dt$$

integrate the eqn w.r.t t

$$\boxed{V_o(t) = -\frac{1}{RC} \int V_i dt}$$

Note: $RC \gg T$ w.r.t. circuit acts as an integrator.


$$V_o = \int_{t_1}^{t_2} V_i(t) dt$$

$$V_o = \int_{t_1}^{t_2} V_i(t) dt + \int_{t_2}^T V_i(t) dt$$

$$V_o = \int_{t_1}^{t_2} V_i(t) dt + \int_{t_2}^T V_i(t) dt - \int_{t_1}^{t_2} V_i(t) dt$$

$$V_o = \int_{t_1}^{t_2} V_i(t) dt + \int_{t_2}^T V_i(t) dt - \int_{t_1}^{t_2} V_i(t) dt$$
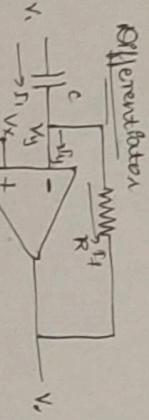
$$V_o = \int_{t_1}^{t_2} V_i(t) dt + \int_{t_2}^T V_i(t) dt - \int_{t_1}^{t_2} V_i(t) dt$$



Apply KCL at node Y
 $I_1 = I_2 + I_3$

$$I_1 = \frac{V_i - V_y}{R}$$


$$C \frac{d(V_i - V_y)}{dt} = \frac{V_y - V_o}{R}$$

$V_x = V_y = 0$ [by virtual ground]


$$C \frac{dV_o}{dt} = -\frac{V_o}{R}$$

$$V_o = -R C \left[\frac{dV_o}{dt} \right]$$

Note $R C \ll T$

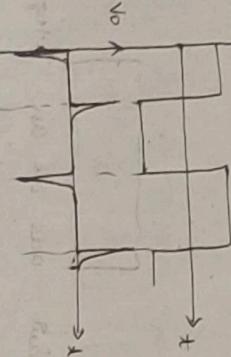

- Design inverting amplifier for $A_v = -5$, sketch i/p o/p waveform for $V_i = 10 \sin \omega t$.
- Design non-inverting amplifier for $A_v = 11$ & sketch i/p and o/p waveform for $V_i = 10 \sin \omega t$.
- For a differentiation.
for $V_i = 10 \sin \omega t$ $\omega = 314$
for an integrator $R_C = 100 \text{ msec}$, sketch i/p & o/p
- For an integrator $V_o = 100 \text{ sin} \omega t$
- Design a circuit using op-amp to get o/p expression.
 $V_o = -(2V_1 + 3V_2 + 4V_3)$
 $\Rightarrow V_o = +(\Delta V_1 + 3V_2 + 4V_3)$
 $\Rightarrow V_o = -(R(V_1 + 3V_2 + 4V_3))$
 $\Rightarrow V_o = +(\Delta V_1 - 3V_2 + 4V_3)$
 $\Rightarrow V_o = R(V_1 - V_2)$

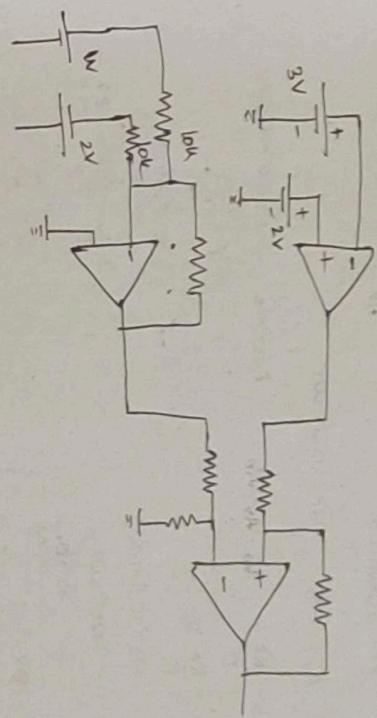

Precision rectifier
Instrumentation amplifier
Square wave or triangular wave generator

Note) Cut-in voltage is

minimum voltage required for the diode to start

conducting and overcome

the barrier potential, hence



regular rectifier do not

rectify a voltage equivalent

to or less than V_F because

it gets the min. potential

required for diode to be a.

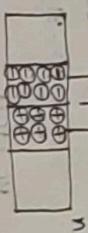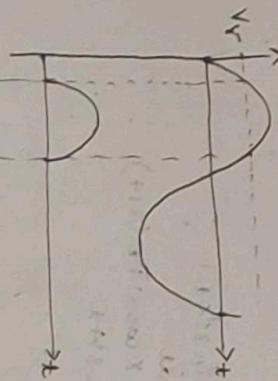


Precision rectifier is a rectifier whose o/p is rectified even if it is less than V_F , very small signals is rectified.

Precision rectifier → half wave rect.

Half wave rectification (Precision)

$V_h = V_b$ (virtual ground)

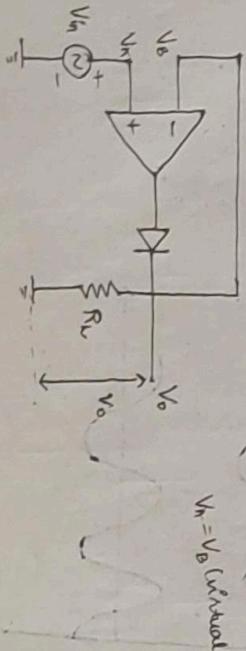


" V_F has no contribution to o/p of the rectifier".


As diode has no effect, one can also assume it is closed path.

During -ve half cycle, diode is reverse biased, hence it does not conduct and hence, o/p voltage is zero.

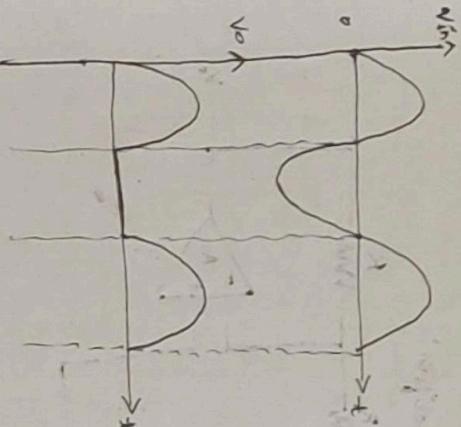When a positive potential is applied, diode is forward biased and conducting, and we obtain a o/p voltage equivalent to V_h .




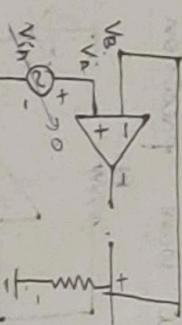At the point, potential is $V_F + V_{sat}$ (V_h). V_h is used to drive the diode thus, obtaining V_h at o/p.



Pulse wave precision rectifier

negative feedback


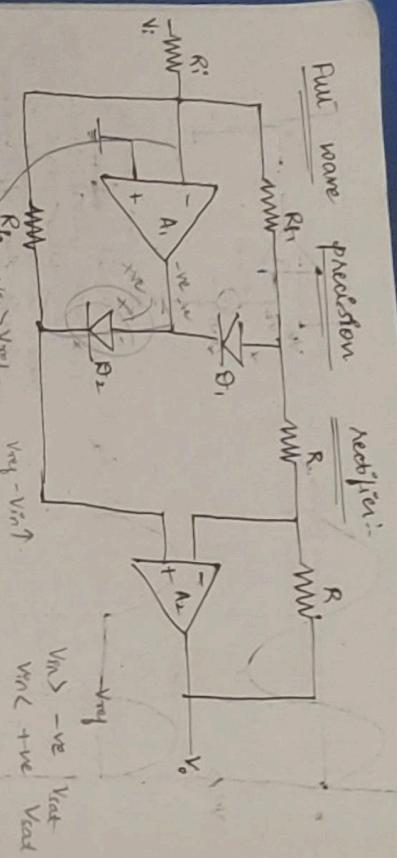


During the wave cycle
if $V_{in} > V_{ref}$
 $V_{out} = -V_{in}$
if $V_{in} < V_{ref}$
 $V_{out} = V_{in}$

terminal is
-Ve, due to which.
 R_1 is forward biased and
 R_2 is reverse biased and not conducting.

" V_{in} has no control over effect on op-amp".

$V_{in} = V_{out}$
(virtual ground)

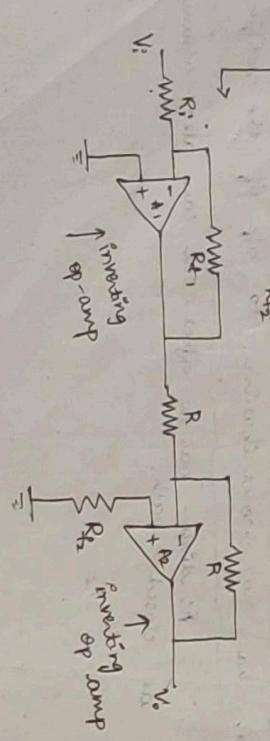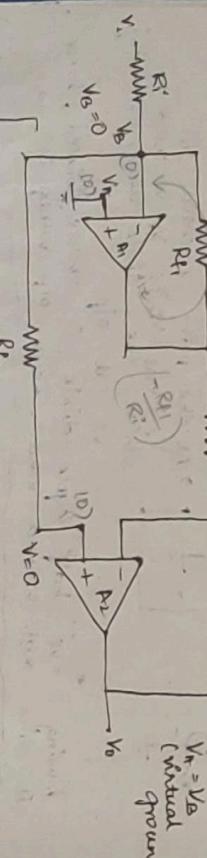

inverting
op-amp

inverting
op-amp

$$\text{Apply KCL at Node } 4$$

$$\frac{V_x}{R_i} + \frac{V_x}{R_1 + R_2 + R_3} + \frac{V_x}{R_2} = 0$$

$$\text{Assume } R_1 = R_2 = R$$

$$\frac{V_x}{R_i} + \frac{3V_x}{2R} = 0$$


$$\text{then } \frac{V_x}{R_i} + \frac{1.5V_x}{R} = 0$$

$$\frac{V_x}{R_i} = -\frac{1.5V_x}{R}$$

$$-\frac{1.5V_x}{R} = \frac{V_x}{R_i}$$


$$V_x = -\frac{V_i R}{R_i (1.5)}$$
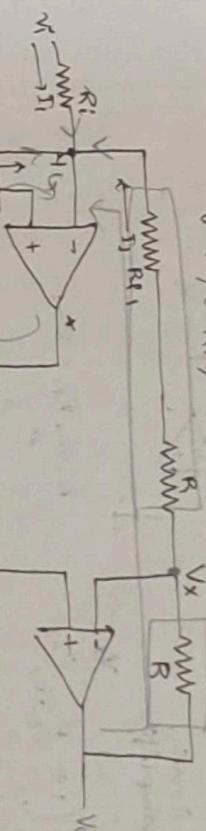
$$\therefore V_x = -\left(\frac{1}{1.5}\right) \left(\frac{R}{R_i}\right) V_i$$



$$V_o = A_{v1} A_{v2} V_i$$
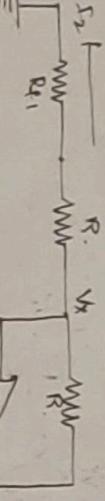
$$V_o = \left(\frac{-R}{R_i}\right) \left(\frac{-R_1}{R_i}\right) V_i = \frac{R_1}{R_i} V_i$$




Non-inverting
amplifier

$$V_o = \left(1 + \frac{R}{R_1 + R}\right) V_x$$

$$V_o = \left(1 + \frac{R}{R_i + R}\right) \left(-\frac{1}{1.5}\right) \frac{R}{R_i} V_i$$

$$= -\left(\frac{R}{1.5}\right) \frac{R}{R_i} V_i$$

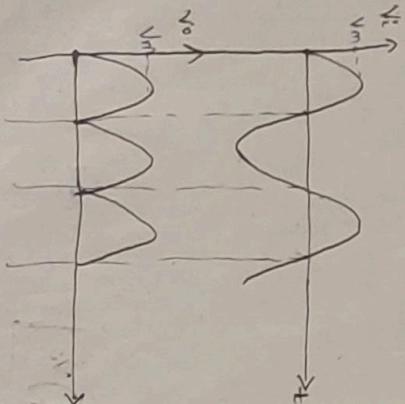This proves that the op-amp is
rectified which may or may not
be amplified depending on R_1, R
and R_i .



Design a full-wave rectifier for a gain of 10.
For a positive half-cycle $R_i = R$ - half cycle
 $V_o = \frac{R_1}{R_i} V_i \rightarrow \text{O}$ $V_o = -\frac{R}{R_i} V_i \rightarrow \text{O}$

Now, let $R_1 = R_2 = R = 10k$


$$\text{then } |AV| = 10$$

$$\textcircled{1} \quad V_o = \frac{R}{R_i} V_i \quad \textcircled{2} \quad V_o = -\frac{R}{R_i} V_i \rightarrow 0$$


$$|K| = R/R_i$$

$$10 = R/R_i \quad A6 = R = 10k$$


Transfer characteristics

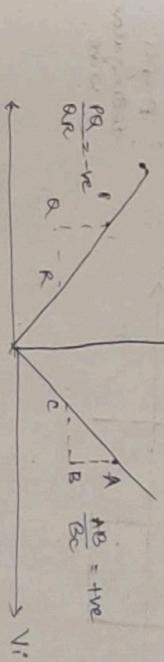

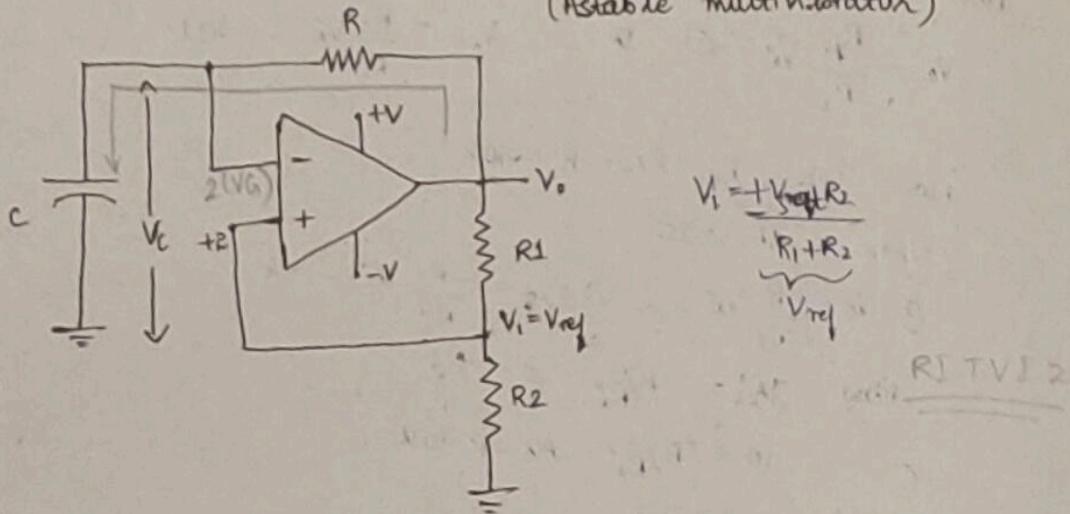Square or triangular wave generator
 (Astable multivibrator)




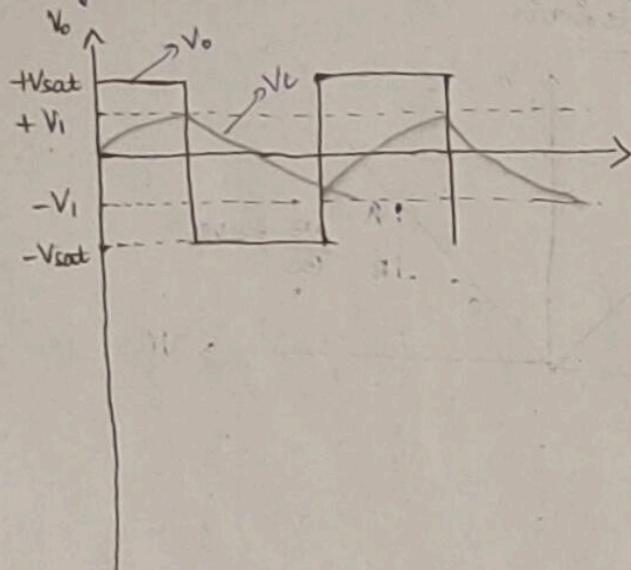Assuming, β is not at the saturation and capacitor is not charged.



R_C should be large to obtain a proper triangular wave

Consider the circuit:

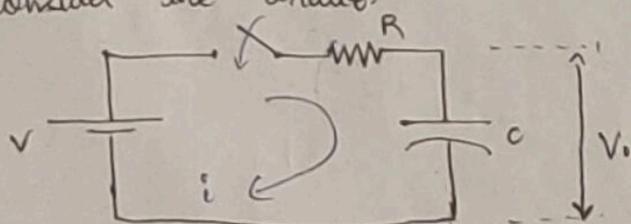

$$\Sigma = C \frac{dV}{dt}$$

$$V = \frac{1}{C} \int \Sigma dt$$



$$+V - i(t)R - \frac{1}{C} \int i(t) dt$$

differentiate wrt to 't'


$$-d_i(t)/dt \cdot R - \frac{1}{C} i(t) \cdot dt = D$$

Square or triangular wave generator

(Astable multivibrator)

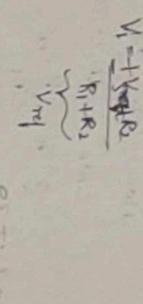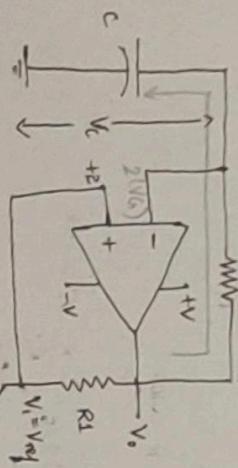

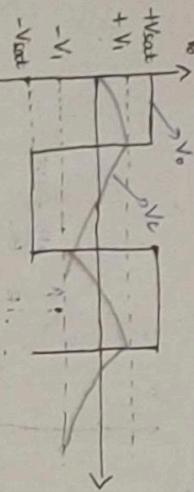Assuming, diode is in saturation and capacitor is not charged.



Rc should be large to obtain a proper rectangular wave


$$V_p = +V_{sat} \quad t_1 = T_{ON}$$

$$V_c(t_1) = +V_1$$

$$V_c(t_1) = V_p - (V_p - V_t)e^{-t_1/Rc}$$

$$\text{Expression for } T_{ON}$$
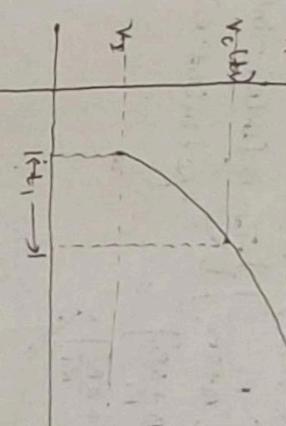
$$V_t = -V_i = -\frac{V_{sat} R_2}{R_1 + R_2}$$




$$V_1 = -V_{sat} - (V_{sat} + \frac{V_{sat} R_2}{R_1 + R_2}) e^{-\frac{T_{ON}}{RC}}, \quad V_{sat} = V_{sat} \left[1 + \frac{R_2}{R_1 + R_2} \right] e^{-\frac{T_{ON}}{RC}}$$

$$\frac{V_{sat} R_1}{R_1 + R_2} = V_{sat} \left[1 - \left(1 + \frac{R_2}{R_1 + R_2} \right) e^{-\frac{T_{ON}}{RC}} \right] e^{-\frac{T_{OFF}}{RC}}$$

$$= V_{sat} - V_{sat} \left[1 + \frac{R_2}{R_1 + R_2} \right] e^{-\frac{T_{OFF}}{RC}}$$

$$I = C \frac{dV}{dt}$$

$$V = \frac{1}{C} \int I dt$$

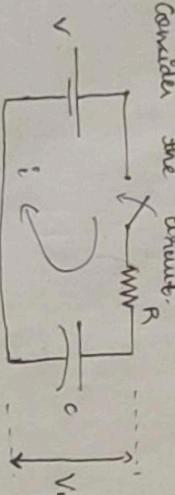

$$-V - I(R) - \frac{1}{C} \int I(t) dt$$

$$\frac{dI(t)}{dt} R - \frac{1}{C} I(t) \cdot dt = D$$

$$\frac{dI(t)}{dt} + \frac{1}{RC} I(t) = 0$$

$$dy/dx + p y = q$$

$$y(x, P) = \int q(x, P) dx$$

$$\int P e^{-P dx} = e^{-P x}$$

$$C = \frac{R}{R_1 + 2R_2}$$

Take 'ln' on both sides

$$-\frac{T_{\text{on}}}{RC} = \ln\left(\frac{R_1}{R_1 + \alpha R_2}\right)$$

$$T_{\text{on}} = RC \ln\left[\frac{R_1}{R_1 + \alpha R_2}\right]$$

$$T_{\text{on}} = RC \ln\left[1 + \frac{\alpha R_2}{R_1}\right]$$

Design a sin-wave generator using op-amp to generate a

frequency of 1kHz.

$$f = \frac{1}{T} = \frac{1}{2RC \ln\left[1 + \frac{\alpha R_2}{R_1}\right]}$$

$$\text{Duty cycle} = \frac{T_{\text{on}}}{T} = \frac{RC \ln\left[1 + \frac{\alpha R_2}{R_1}\right]}{2RC \ln\left[1 + \frac{\alpha R_2}{R_1}\right]} = \frac{1}{2} = 0.5\% = 50\%$$

$$T_{\text{off}} = RC \ln\left(1 + \frac{\alpha R_2}{R_1}\right)$$

$$T = T_{\text{on}} + T_{\text{off}}$$

$$= 2RC \ln\left(1 + \frac{\alpha R_2}{R_1}\right)$$

$$V_L = V_i = \frac{+V_{\text{sat}} R_2}{R_1 + R_2}, \quad V_p = -V_{\text{sat}}, \quad t_i = T_{\text{off}}$$

$$V_i(t_i) = -V_i = -\frac{V_{\text{sat}} R_2}{R_1 + R_2}$$

$$V_i(t_i) = V_i - (V_i - V_p)e^{-t_i/T_{\text{off}}/RC}$$

$$-V_i = -V_{\text{sat}} - \left(-V_{\text{sat}} + \frac{V_{\text{sat}} R_2}{R_1 + R_2}\right)e^{-t_i/T_{\text{off}}/RC}$$

$$-V_{\text{sat}} R_2 = -V_{\text{sat}} - V_{\text{sat}} \left[1 + \frac{R_2}{R_1 + R_2}\right] e^{-t_i/T_{\text{off}}/RC}$$

$$\frac{V_{\text{sat}} R_2}{R_1 + R_2} = V_{\text{sat}} \left[1 + \frac{[R_1 + R_2 + R_2]}{R_1 + R_2}\right] e^{-t_i/T_{\text{off}}/RC}$$

$$\ln\left[1 + \frac{\alpha R_2}{R_1}\right] = 5$$

exponential on both sides

$$1 + \frac{\alpha R_2}{R_1} = e^5$$

$$1 + \frac{\alpha R_2}{R_1} = 174$$

$$\frac{\alpha R_2}{R_1} = 173$$

$$\frac{R_2}{R_1} = \left(\frac{173}{100}\right)^{1/5}$$

$$\frac{R_2}{R_1} = 1.40647$$

$$\frac{R_2}{R_1 + R_2} = \frac{-T_{\text{off}}/RC}{R_1 + R_2}$$

$$\frac{R_2}{R_1 + R_2} = \frac{R_1 + R_2 - R_1 C}{R_1 + R_2}$$

We have square triangular wave generator



$$(1 + \frac{R_2}{R_1}) = e = 2.7183$$

$$T_{on} = T_{off} = R_C C \ln(e)$$

$$f = \frac{1}{T} = \frac{1}{2RC}$$

$$R_a = \frac{2.7183 - 1}{2} = 0.8591$$

$$R_2 = 10k \quad R_1 = 8.591k$$

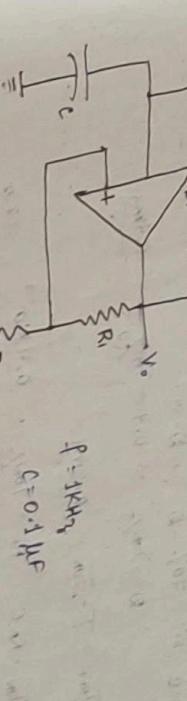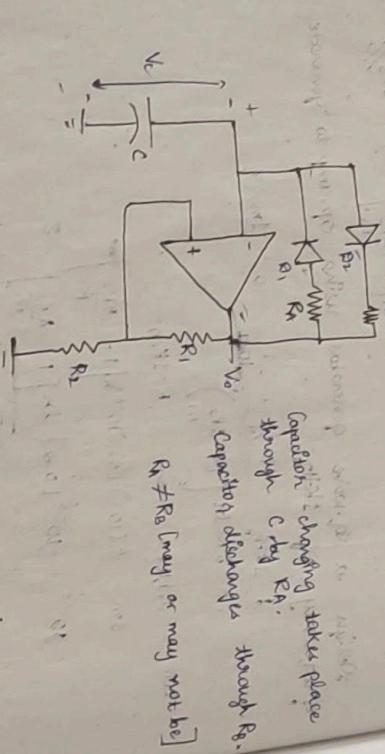

Design a free running oscillator which generates a frequency of 50 Hz and has a wave (50°) 50° and wave (10°) 40°.

$$T = R_C C$$

$$f = \frac{1}{T} = \frac{1}{(R_C + R_B)C}$$

$$D = \frac{R_a}{R_a + R_B}$$

$$R_a/R_B > 0.4591 \quad (1 + \frac{R_2}{R_1}) = e$$

$$T_{on} = R_a C$$

$$T_{off} = R_B C$$

$$\theta = 50^\circ$$

$$\phi = 40^\circ$$

$$\alpha = 30^\circ$$

$$\beta = 50^\circ$$

$$\gamma = 40^\circ$$

$$\delta = 30^\circ$$

$$\epsilon = 50^\circ$$

$$\zeta = 40^\circ$$

$$\eta = 30^\circ$$

$$\text{We have } T = \frac{1}{f} = \frac{1}{10^3} = 1 \text{ ms}$$

$$T = T_{on} + T_{off}$$

$$T_{on} = R_a C \ln\left(\frac{1+R_2/e}{R_1}\right) \quad T_{off} = R_B C \ln\left(\frac{1+R_2/e}{R_1}\right)$$

$$\text{Let } \frac{1+R_2/e}{R_1} = e. \quad \therefore R_2 = e R_1$$

$$\therefore T_{on} = R_a C$$

$$T_{off} = R_B C$$

$$\text{Given } \theta = 30^\circ. \quad \therefore \frac{0.3}{0.7} = \frac{T_{on}}{T_{off}}$$

$$\theta = \frac{T_{on}}{T} \approx 0.3 = \frac{0.3}{10^{-3}} = 0.3 \text{ ms}$$

$$T_{off} = T - T_{on} = (1 - 0.3) \text{ ms} = 0.7 \text{ ms}$$

$$0.3 \times 10^{-3} = R_a (0.1 \times 10^{-6}) \quad \therefore 0.7 \times 10^{-3} = R_B (0.1 \times 10^{-6})$$

$$R_a = 3 k\Omega$$

$$T_{on} = R_a C \ln\left(1 + \frac{R_2}{R_1}\right)$$

$$T = (R_a + R_B) C \ln\left(1 + \frac{R_2}{R_1}\right)$$

$$f = \frac{1}{T} = \frac{1}{(R_a + R_B) C \ln\left(1 + \frac{R_2}{R_1}\right)}$$

$$\text{Duty cycle} = \frac{T_{on}}{T} = \frac{R_a}{R_a + R_B}$$

Depending on ratio of R_a & R_B , Duty cycle may be more than equal to 50% less than 50%

case 50% = θ $\theta = 0.5$

$$\theta = \frac{T_{on}}{T} \Rightarrow 0.5 = \frac{T_{on}}{10^{-3}}$$

$$T_{on} = \underline{0.5ms}$$

$$T_{off} = T - T_{on} = \underline{0.5ms}$$

$$T_{on} = R_a C \quad R_a = \frac{T_{on}}{C} = \frac{0.5 \times 10^{-3}}{0.1 \times 10^{-6}} = 5K\Omega$$

$$R_a = 5K\Omega \quad \frac{0.5 \times 10^{-3}}{0.1 \times 10^{-6}} = 5K\Omega$$

$$case \theta = 40\% = \theta \quad \theta = 0.4$$


$$\theta = T_{on}/T \Rightarrow 0.4 = \frac{T_{on}}{10^{-3}} = \underline{0.4ms}$$

$$T_{off} = T - T_{on} = \underline{0.3ms}$$

$$T_{on} = R_a C \quad R_a = \frac{T_{on}}{C} = \frac{0.4 \times 10^{-3}}{0.1 \times 10^{-6}} = \underline{4K\Omega}$$

$$T_{off} = R_a C \quad R_a = \frac{T_{off}}{C} = \frac{0.6 \times 10^{-3}}{0.1 \times 10^{-6}} = \underline{6K\Omega}$$

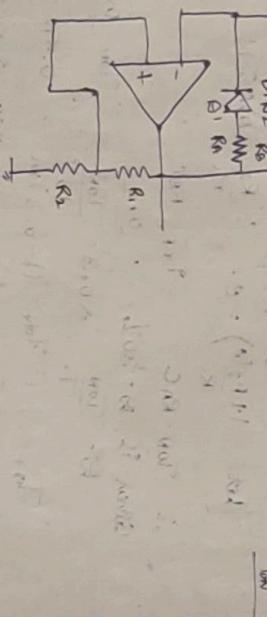Design a square wave generator using op-amp. and generate a frequency of $5KHz$ with an time ratio that of T_{off} . Assume $R_1 = R_2 = 10K\Omega$, $C = 0.1\mu F$



$$f = 5kHz$$

$$T = \frac{1}{5 \times 10^3} = \underline{0.0ms}$$

$$T = T_{on} + T_{off}$$

$$T = 3T_{off}$$

$$T_{off} = \frac{0.8 \times 10^{-3}}{3} = \underline{0.67ms}$$

$$T_{on} = 2T_{off} = \underline{1.333ms}$$

$$\theta = \frac{T_{on}}{T} = 0.6666 = \underline{66.66\%}$$

$$R_a = T_{on} = R_a C \ln \left(1 + \frac{\theta R_2}{R_1} \right)$$

$$183.33 \times 10^{-6} = R_a (0.1 \times 10^{-6}) \ln \left[1 + 2 \frac{(10k\Omega)}{4k\Omega} \right]$$

$$R_a = \frac{183.33 \times 10^{-6}}{0.1 \times 10^{-6} \ln(3)} = 1.8136 K\Omega$$


$$R_B = T_{off} = R_B C \ln \left(1 + \frac{\theta R_2}{R_1} \right)$$

$$66.664 \times 10^{-6} = R_B (0.1 \times 10^{-6}) \ln \left(1 + \frac{6.664 \times 10^{-6}}{0.1 \times 10^{-6} \ln(3)} \right)$$

$$R_B = \frac{66.664 \times 10^{-6}}{0.1 \times 10^{-6} \ln(3)} = \underline{0.6068 K\Omega}$$

Instrumentation amplifier

Instrument system

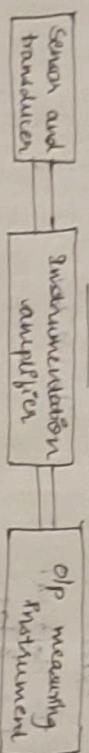

S.I.A. should share op impedance and high CMRR due to reducing noise from the environment.
Example (transducer)




When bridge is balanced
(i.e., $R_a R_b = R_c R_d$)

$$V_1 - V_2 = 0$$

$$\textcircled{3} \quad V_1 = V_2$$

$$V_1 - V_2 = \frac{R_a}{R_a} (V_1 - V_2) = 0$$

Instrumentation amplifier

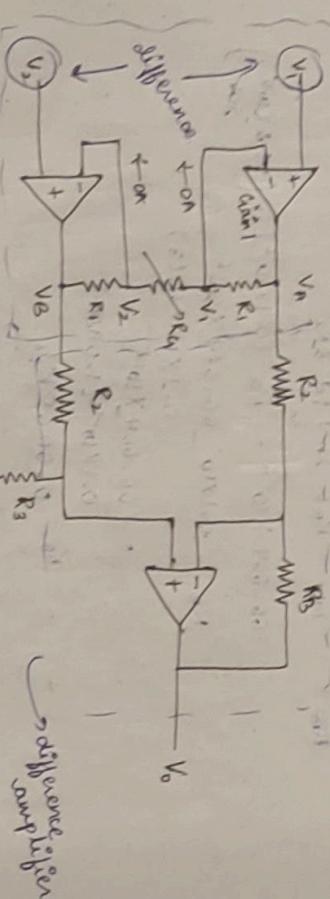

Note: amplifier where op is connected should have high CMRR to avoid noise.

$$V_h - V_B = A_v(V_1 - V_2)$$

current across resistors in series is constant

$$I = \frac{V_h - V_1}{R_1} = \frac{V_1 - V_2}{R_2} = \frac{V_2 - V_B}{R_3}$$

$$\text{case i) } \frac{V_h - V_1}{R_1} = \frac{V_1 - V_2}{R_2}$$

$$V_h - V_1 + \frac{R_1}{R_2}(V_1 - V_2) = 0$$

$$V_h - V_1 + \frac{R_1}{R_2} V_1 - \frac{R_1}{R_2} V_2 \Rightarrow V_h = \frac{R_1}{R_2} V_2 + V_2 \left(1 + \frac{R_1}{R_2} \right) \rightarrow 0$$

$$V_2 - V_B = \frac{R_1}{R_2} (V_1 - V_2)$$

$$V_2 - \frac{R_1}{R_2} (V_1 - V_2) = V_B \quad \text{and} \quad V_2 = V_B + V_1 \frac{R_1}{R_2} = \frac{R_1}{R_2} V_1$$

$$V_o = \frac{R_3}{R_2} (V_B - V_A)$$

$$= \frac{R_3}{R_2} \left[V_2 \left(1 + \frac{R_1}{R_2} \right) - \frac{R_1}{R_2} V_1 \right] - \left[\frac{R_3}{R_2} V_2 + V_1 \left(1 + \frac{R_1}{R_2} \right) \right]$$

$$= \frac{R_3}{R_2} \left\{ V_2 \left[1 + \frac{R_1}{R_2} \right] - \frac{R_1}{R_2} V_1 + \frac{R_1}{R_2} V_2 - V_1 \left[1 + \frac{R_1}{R_2} \right] \right\}$$

$$= \frac{R_3}{R_2} \left\{ \left(1 + \frac{R_1}{R_2} \right) (V_2 - V_1) + \frac{R_1}{R_2} (V_2 - V_1) \right\}$$

$$= \frac{R_3}{R_2} (V_2 - V_1) \left[1 + \frac{2R_1}{R_2} \right]$$

$$V_o = \frac{R_3}{R_2} (V_2 - V_1) \left[1 + \frac{2R_1}{R_2} \right]$$

$$A_v = \frac{V_o}{V_2 - V_1} = \frac{R_3}{R_2} \left[1 + \frac{2R_1}{R_2} \right]$$

v.v.

v.v.


$$I = \frac{V_h - V_1}{R_1} = \frac{V_1 - V_2}{R_2} = \frac{V_2 - V_B}{R_3}$$

R_a and R_b , suitable resistors would be enough to control the required gain. Reducing value of R_a , gain can be adjusted. Usually (R_1, R_2, R_b) are fixed. R_a is variable.

Design an instrumentation amplifier for a gain 11.

$$Av = \frac{V_o}{V_2 - V_1} = \frac{R_3}{R_2} \left[1 + \frac{R_1}{R_a} \right]$$
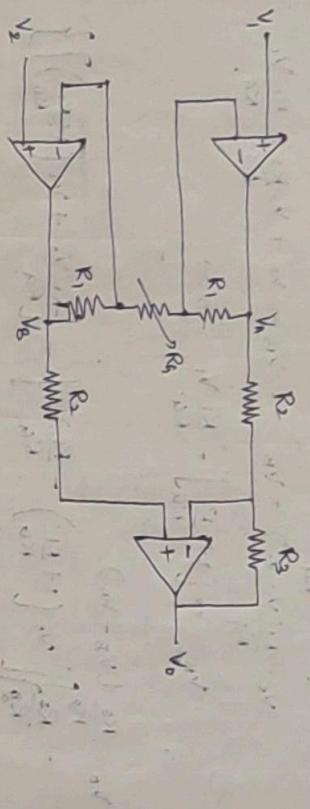
$$\text{Let } R_1 = R_2 = R_3 = R_a = 10\text{ k}\Omega \quad (\text{Assume})$$



$$11 = \frac{10k}{10k} \left[1 + \frac{10k}{10k} \right]$$

$$11 = \left[1 + 1 \right] \cdot 10 \Rightarrow 11 = 2 \cdot 10 \Rightarrow 11 = 20$$

$$R_4 = \frac{200k}{10} = 20k$$

$$R_a = 10k \quad \text{OK}$$

$$10 = 2(10k) \Rightarrow 10 = 20k \Rightarrow k = 0.5$$

$$R_1 = R_2 = 10k \Omega$$

$$1 + \frac{R_1}{R_a} = 11 \Rightarrow 1 + \frac{10k}{10} = 11 \Rightarrow k = 1$$

$$1 + \frac{R_1}{10k} = 11 \Rightarrow 1 + \frac{10}{10} = 11 \Rightarrow k = 1$$


$$R_1 = \frac{10 \times 10k}{10} = 100k \Omega$$

R_a and R_e , suitable resistors would be enough to control the required gain. Reducing value of R_a , gain can be adjusted. Usually R_1, R_2, R_g are fixed. R_a is variable.

Design an instrumentation amplifier for a 11 gain.

$$A_V = 11 \quad A_V = \frac{V_o}{V_s - V_i} = \frac{R_2}{R_1} \left[1 + \frac{R_1}{R_a} \right]$$
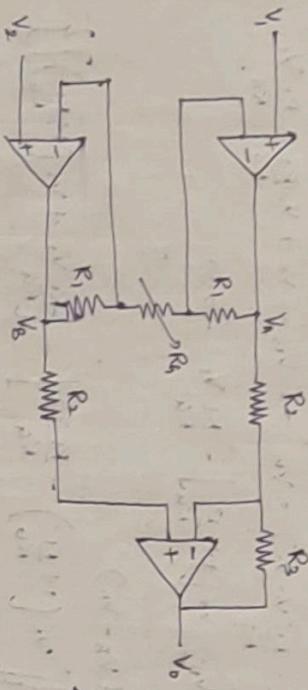
$$\text{Let } R_1 = R_2 = R_g = R_a = 10\text{ k}\Omega \quad (\text{Assume})$$



$$11 = \frac{10k}{10k} \left[1 + \frac{10k}{10k} \right]$$

$$10 = 2(10k)$$

$$R_a = \frac{2(10k)}{10} = \underline{\underline{2k\Omega}}$$

OR:

$$\text{Let } R_1/R_2 = 1 \quad \text{and} \quad R_g = 10\text{ k}\Omega$$

$$1 + \frac{R_1}{R_2} = 11 \quad \therefore \quad 1 + \frac{R_1}{R_a} = 11$$

$$1 + \frac{R_1}{10k} = 11$$

$$R_1 = \frac{10k \times 10k}{11} = \underline{\underline{50k\Omega}}$$

555 timer

Monostable

The op is constant

in two states, we have

Based on number of stable states


unstable (zero stable state) multivibrator

\Rightarrow Monostable (one stable state) multivibrator

unstable (two stable state) multivibrator

Astable is also called free running oscillator.


Astable Multivibrator

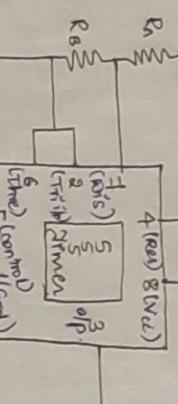

capacitor C_2 to cancel the noise
($2/3$ of VCC)

S - Control $\text{Op} = \frac{2}{3}$ of VCC

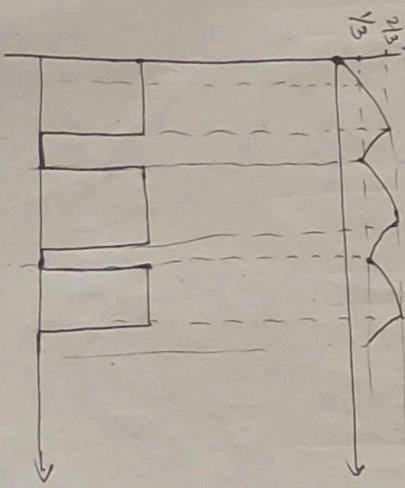- 5 - control [digital input]
- 8 - VCC
- 1 - Gnd
- 4 - Reset
- 7 - Discharge
- 2 - Trigger Op
- 6 - Threshold.



charging time constant = $\tau = (R_A + R_B)C$
discharge time constant = $\tau = (R_A + R_B)C$

stage 6) capacitor voltage = $\frac{2}{3}$ rd of VCC or greater (less than $\frac{2}{3}$)


then, trigger $\text{Op} > \text{Vcc}$

threshold < 5 (forward Op)

$\therefore C_1 = 0$, $C_2 = 0$, no change than previous state
[previous its voltage is zero.
then, 2 and 5 depends on it (trigger Op , threshold)
then, 2 and 5 depends on it (trigger Op , threshold)]

$\therefore R = 0$ as $C_1 = 0$, $S = 1$ as $C_2 = 1$, $\bar{Q} = 1$, $\bar{R} = 0$
 $\text{Op} = 1$, transistor (discharge R_C or Q)

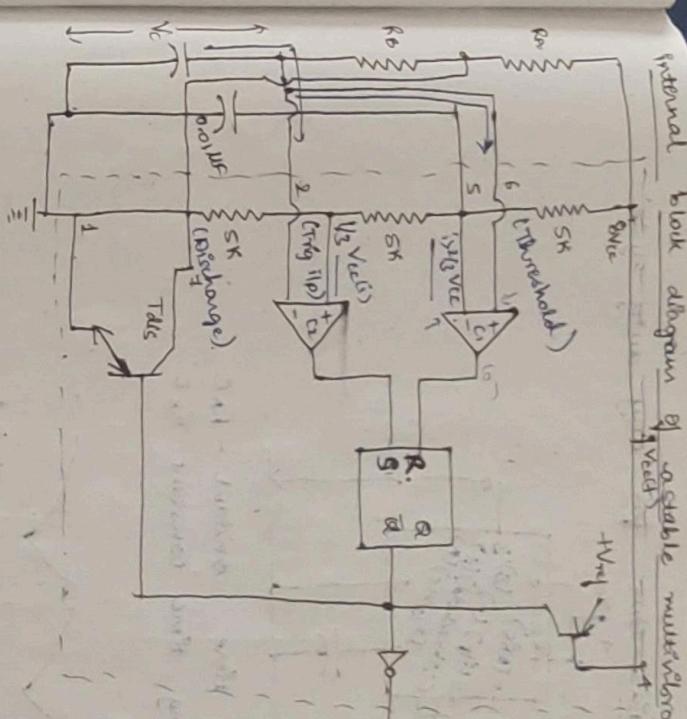charge (Op) capacitor voltage is $\frac{2}{3}$ rd of V_{CC}
the (2) $\text{Op} > \frac{2}{3} V_{CC}$, then $C_2 = 0$, $\bar{Q} = 0$.
5 (threshold) > 5 (forward Op), then $C_1 = 1$, $R = 1$, $\bar{Q} = 1$.
transistor (discharge) is on - 1, capacitor sta




changing time constant = $(R_A + R_B)C$

discharging time constant = $(R_A + R_B)C$


transistor (NPN) depends on \bar{Q} acting as switch.

Stable oscillation for any duty cycle:-

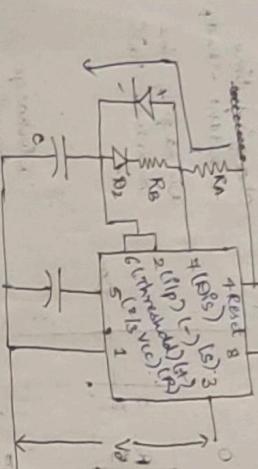

Changing time constant - $R_A C$
Exchanging time constant - $R_B C$

Output expressn

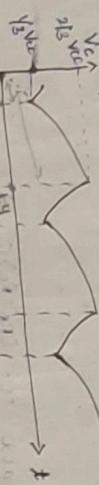

(N.E.H.A.D. diode)

$$\text{to find } t_{q1} = \frac{\ln(1 - e^{-t_q/(R_A + R_B)C})}{(R_A + R_B)C} \quad V_{C1}(t_q) = V_{cc}(1 - e^{-t_q/(R_A + R_B)C})$$

$$\frac{2}{3}V_{cc} = V_{cc}(1 - e^{-t_q/(R_A + R_B)C})$$

$$e^{-t_q/(R_A + R_B)C} = 1 - \frac{2}{3} = \frac{1}{3}$$

t_q

on b.s.

$t_{q1} =$

$0.40546 (R_A + R_B)C$

$$\text{to find } t_{q2} = \frac{\ln(1 - e^{-t_q/(R_A + R_B)C})}{(R_A + R_B)C} = \ln(1/3) = -1.0986$$

t_{q2}

on b.s.

$t_{q2} =$

$0.40546 (R_A + R_B)C$


changing time constant $= T_{ON} = R_B C$

Exchanging time constant $= T_{OFF} = R_A C$

$$T = T_{ON} + T_{OFF} = 0.913(R_A + R_B)C + 0.693(R_B)C$$

$$\frac{T}{T} = \frac{0.913(R_A + R_B)C + 0.693(R_B)C}{0.693(R_A + R_B)C} = 1.343$$

Similarly $T_{OFF} = 0.693 R_B C$

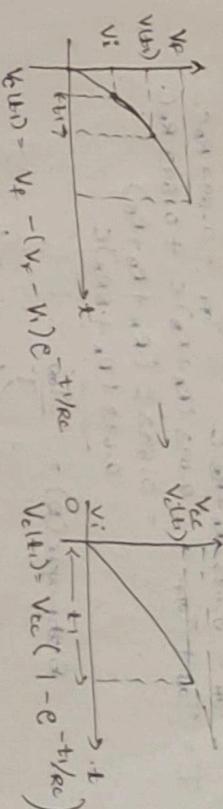

$t_{q1} =$

$0.40546 (R_A + R_B)C$

t_{q2}

on b.s.

$t_{q2} =$

$0.40546 (R_A + R_B)C$

$$\begin{aligned}T_{ON} &= 0.693 (R_A + R_B) C & T_{OFF} &= 0.693 R_C \\T &= T_{ON} + T_{OFF} = 0.693 (R_A + R_B) C + 0.693 R_C \\&= 0.693 C (R_A + R_B + R_C) \\&\Rightarrow 0.693 \frac{(R_A + R_B) C}{R_A + R_B + R_C}\end{aligned}$$


$$\text{Duty cycle (D)} = \frac{T_{ON}}{T}$$

$$= \frac{0.693(R_A + R_B)C}{0.693(R_A + R_B + R_C)C}$$

$$D = \frac{R_A + R_B}{R_A + R_B + R_C}$$

$$f = \frac{1}{T} = \frac{1}{0.693(R_A + 2R_B)C}$$

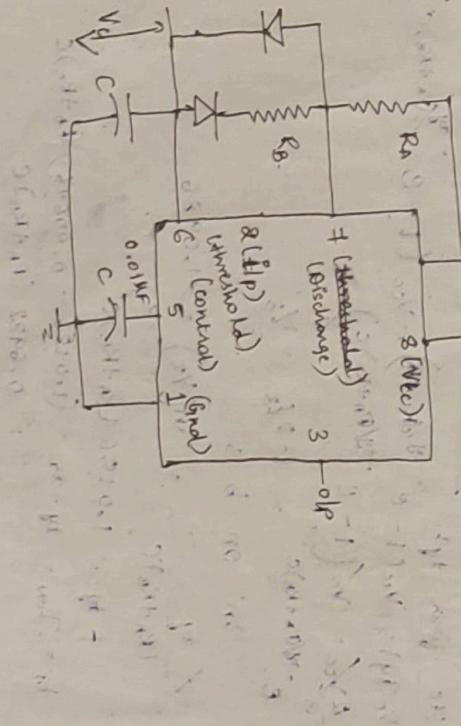Astable multivibrator for any duty cycle.



Design available multivibrator using 555 timer for

following specification

$$f = 1 \text{ KHz}, D = 50\%$$

$$f = 1 \text{ KHz}, D = 25\%$$

$$f = 1 \text{ KHz}, D = 45\%$$

$$\text{Given } f = 1 \text{ KHz} \\ T = 1/4 - \frac{1}{10^3} = 10^{-3} = \underline{\underline{1 \text{ ms}}}$$

$$D = 50\% = 0.5 \\ D = \frac{T_{on}}{T} \Rightarrow 0.5 \times T = T_{on}$$

$$T_{on} = 0.5 \times 10^{-3} = \underline{\underline{0.5 \text{ ms}}}$$

$$T_{off} = T - T_{on} \\ = \underline{\underline{0.5 \text{ ms}}}$$


$$R_a = 0.693(R_a)C \quad \text{Assume} \\ C = 0.1 \mu F$$

$$R_a = \frac{0.5 \times 10^{-3}}{0.693 \times 10^{-6}} = \\ \underline{\underline{0.693 \times 0.1 \times 10^6}}$$

$$R_a = 1.0215 \text{ k}\Omega$$

$$T_{on} = T_{off} = R_a = 1.0215 \text{ k}\Omega$$
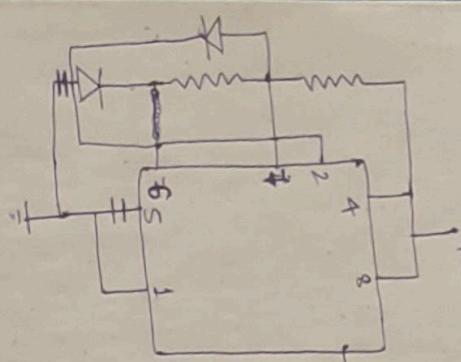
$$= \underline{\underline{1.02 \text{ k}\Omega}}$$



$$R_a = 3.6045 \text{ k}\Omega$$

$$T_{off} = 0.693 R_a C$$

$$R_a = \frac{T_{off}}{0.693 C} = \frac{0.45 \times 10^{-5}}{0.693 \times 0.1 \times 10^{-6}} = \\ \underline{\underline{6.93 \times 10^5}}$$

$$R_a = 10.8025 \text{ k}\Omega$$

$$\text{Given } f = 1 \text{ KHz} \\ T = 1/4 - \frac{1}{10^3} = 10^{-3} = \underline{\underline{1 \text{ ms}}}$$

$$D = 25\% = 0.25$$

$$D = \frac{T_{on}}{T} \Rightarrow 0.25 \times T = T_{on}$$

$$T_{on} = 0.25 \times 10^{-3} = \underline{\underline{0.25 \text{ ms}}}$$

$$T_{off} = T - T_{on} \\ = \underline{\underline{0.75 \text{ ms}}}$$

$$T_{on} = 0.693 R_a C$$

$$T_{off} = 0.693 R_a C$$

$$\text{Assume } C = 0.1 \mu F \\ T_{on} = 0.693 R_a C \\ R_a = \frac{T_{on}}{0.693 C} = \frac{0.45 \times 10^{-3}}{0.693 \times 0.1 \times 10^{-6}} = \underline{\underline{6.5 \times 10^5}}$$

$$T_{off} = T - T_{on} = (1 + 0.25) \text{ ms} = \underline{\underline{0.75 \text{ ms}}}$$

$$T_{off} = 0.693 R_a C \\ R_a = \frac{T_{off}}{0.693 C} = \frac{0.75 \times 10^{-3}}{0.693 \times 0.1 \times 10^{-6}} = \underline{\underline{1.05 \times 10^5}}$$

$$R_a = 1.05 \times 10^5 \text{ k}\Omega$$

Design astable multivibrator for 555 timer without diode
for following specification

$$f = 1 \text{ KHz}, D = 70\%$$

$$f = \frac{1}{T} \Rightarrow T = \frac{1}{f} = \frac{1}{10^3} = 10^{-3} = 1 \text{ ms}$$

$$D = \frac{T_{ON}}{T} \Rightarrow 0.7 = \frac{T_{ON}}{1 \text{ ms}}$$

$$T_{ON} = D \times T = 0.7 \times 10^{-3} = 0.7 \text{ ms}$$

$$T_{OFF} = T - T_{ON} = (1 - 0.7) \text{ ms} = 0.3 \text{ ms}$$

$$T_{ON} = 0.693(R_A + R_B)C$$

$$T_{OFF} = 0.693R_B C \quad (\text{Assume } C = 0.1 \mu\text{F})$$

$$0.8 \text{ ms} = 0.693 R_B (0.1 \times 10^{-6})$$

$$R_B = \frac{0.8 \times 10^6}{0.693 \times 0.1 \times 10^{-6}}$$

$$R_B = \underline{\underline{4.829 \text{ k}\Omega}}$$

$$T_{ON} = 0.693 R_A C + \underline{\underline{0.693 R_B C}}$$

$$0.7 \text{ ms} = 0.693 R_A C + 0.3 \text{ ms}$$

$$0.693 R_A C = (0.7 - 0.3) \times 10^{-3}$$

$$R_A = \frac{0.4 \times 10^{-3}}{0.693 \times 0.1 \times 10^{-6}} = \underline{\underline{5.772 \text{ k}\Omega}}$$