
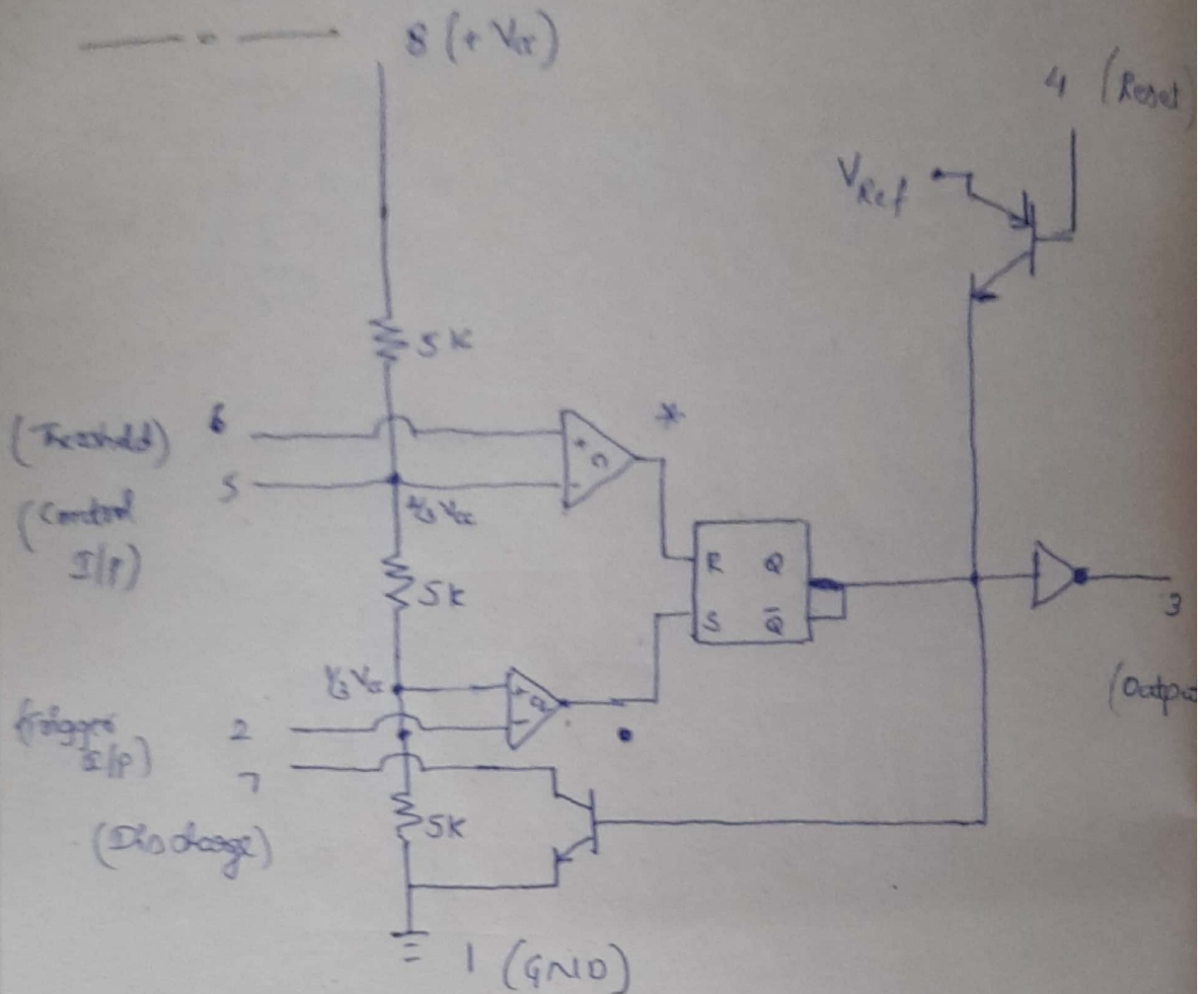


Unit 5: Linear ICs

555 Timer

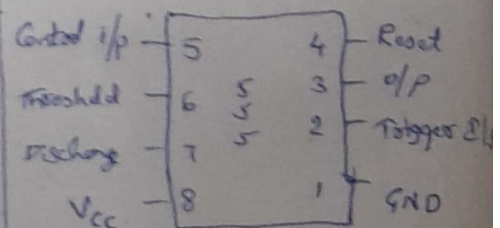

R	S	Q	\bar{Q}	
0	0	Q	\bar{Q}	No change
0	1	1	0	Set
1	0	0	1	Reset
1	1	0*	0*	Invalid



- $\text{Trigger i/p} > \frac{1}{3} V_{cc} \rightarrow 0$ (S)
- $\text{Trigger i/p} < \frac{1}{3} V_{cc} \rightarrow 1$
- $\text{Threshold} > \frac{2}{3} V_{cc} \rightarrow 1$ (R)
- $\text{Threshold} < \frac{2}{3} V_{cc} \rightarrow 0$

⇒ when Trigger $i/p < 1/3 V_{cc}$ → set pin in High (1)

Output is High (1), discharge transistor is $\frac{Q}{1}$
(0)

⇒ when Threshold $i/p > 2/3 V_{cc}$

then $R = 1$

then $Q = 0$, $\bar{Q} = 1$

Output = $\frac{0}{2}$ ^{empt}



discharge transistor is ON (1)

→ In pnp transistor 4 pin V_{cc} is 0 then transistor off


Multivibrator (Using 555 Timer)

- Astable Multivibrator (zero stable state)
- Monostable Multivibrator (one stable state)
- Bistable Multivibrator (two stable state)

Astable Multivibrator

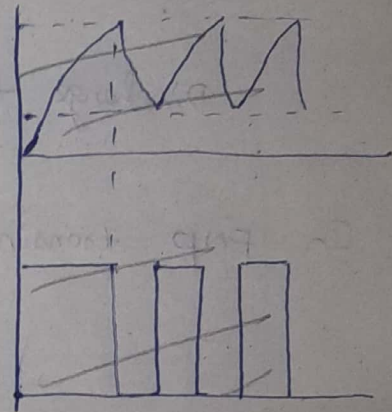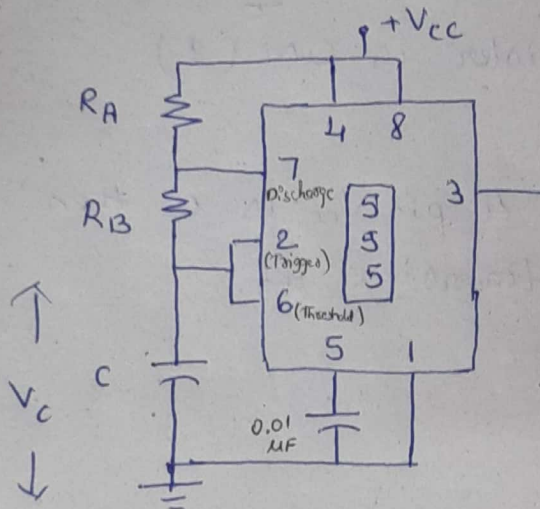


Internal


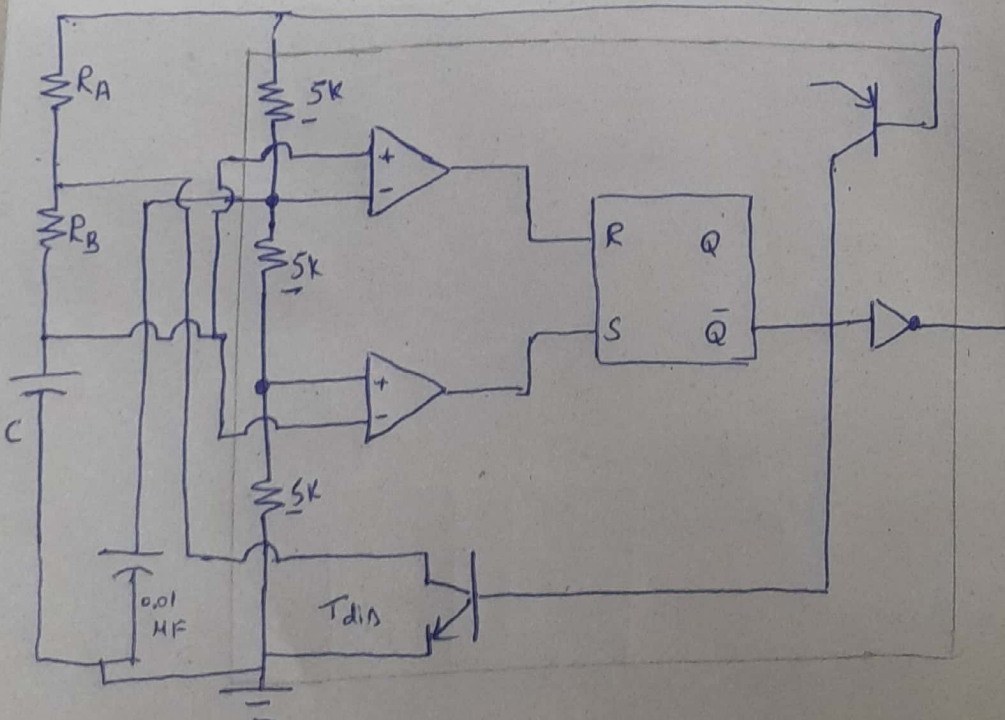


* charging Time const = $(R_A + R_B)C$


Discharging time const = $R_B C$

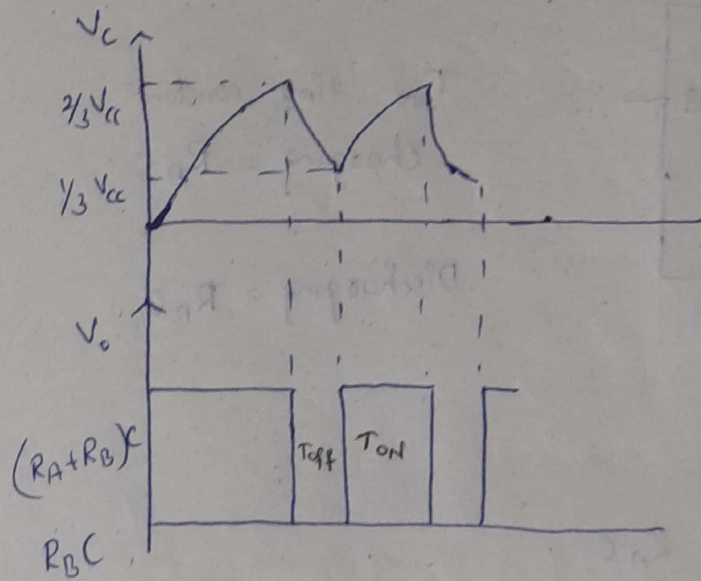


Astable Multivibrator using 555 Timer

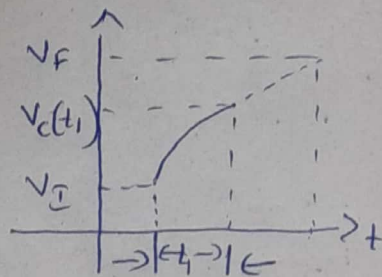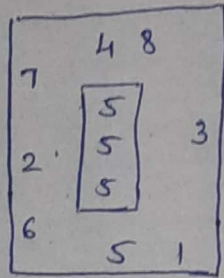
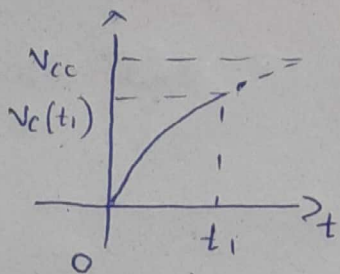
$$V_c(t_1) = V_F - (V_F - V_I) e^{-t_1/RC}$$



$$V_c(t_1) = V_{cc} (1 - e^{-t_1/RC})$$

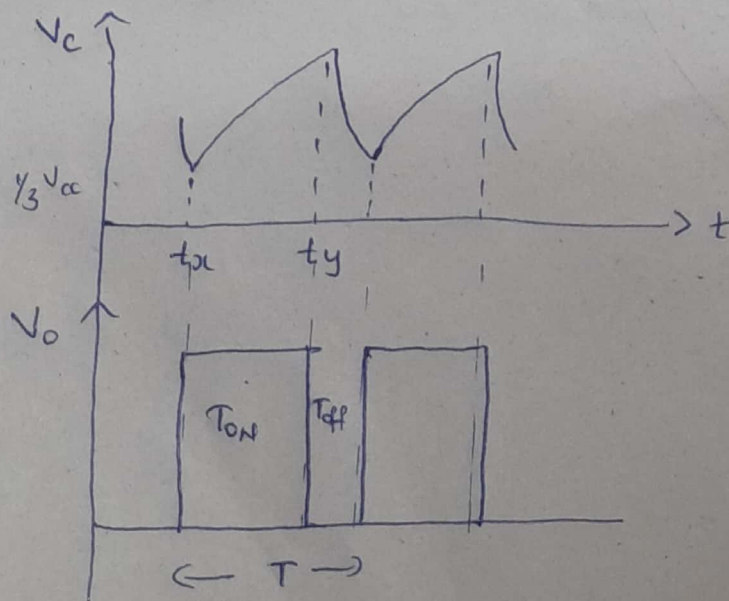

charging time constant $= (R_A + R_B)C$

Discharging $= R_B C$

To find t_x

$$V_c(t_x) = V_{cc} \left(1 - e^{\frac{-t_x}{(R_A + R_B)C}} \right)$$

$$\frac{1}{3} V_{cc} = V_{cc} \left(1 - e^{\frac{-t_x}{(R_A + R_B)C}} \right)$$

$$\cancel{V_{cc}} e^{\frac{-t_x}{(R_A + R_B)C}} = \frac{1}{3} - 1 = \cancel{-} \frac{2}{3}$$

$$\cancel{V_{cc}} \frac{t_x}{(R_A + R_B)C} = \ln\left(\frac{2}{3}\right) = \cancel{-} 0.4054$$

$$\boxed{t_x = 0.4054 (R_A + R_B)C}$$

to find t_y

$$V_c(t_y) = V_{cc} \left(1 - e^{\frac{-t_y}{(R_A + R_B)C}} \right)$$

$$\frac{2}{3} V_{cc} = V_{cc} \left(1 - e^{\frac{-t_y}{(R_A + R_B)C}} \right)$$

$$\cancel{V_{cc}} e^{\frac{-t_y}{(R_A + R_B)C}} = \frac{2}{3} - 1 = \cancel{-} \frac{1}{3}$$

$$\cancel{V_{cc}} \frac{t_y}{(R_A + R_B)C} = \ln\left(\frac{1}{3}\right) = \cancel{-} 1.0986$$

$$t_y = 1.0986 (R_A + R_B) C$$

$$T_{ON} = t_y - t_x$$

$$T_{ON} = 0.693 (R_A + R_B) C$$

$$T_{off} = 0.693 R_B C$$

$$T = T_{ON} + T_{off} = 0.693 (R_A + 2R_B) C$$


$$\text{Duty Cycle} = \frac{T_{ON}}{T} = \frac{0.693 (R_A + R_B) C}{0.693 (R_A + 2R_B) C}$$

$$\text{Duty Cycle} = \frac{R_A + R_B}{R_A + 2R_B}$$

$$f = \frac{1}{T} = \frac{1}{0.693 (R_A + 2R_B) C}$$

Design Astable MV using 555 timer for following specification

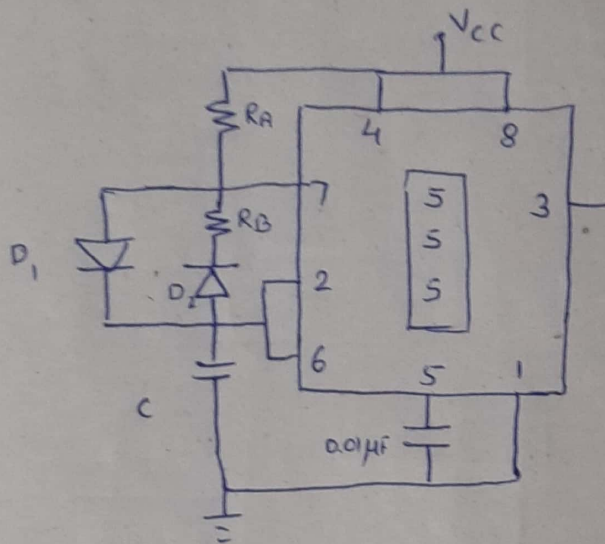- (i) $f = 1 \text{ KHz}$, 50% Duty cycle
- (ii) $f = 1 \text{ KHz}$, 75% Duty cycle
- (iii) $f = 1 \text{ KHz}$, Duty cycle = 25%



$$(i) T = \frac{1}{f} = 1 \text{ ms}$$

$$\text{Duty cycle} = \frac{T_{ON}}{T} \quad \therefore T_{ON} = 0.5 \times 1 \times 10^{-3} \\ = 0.5 \text{ ms}$$

$$T = T_{ON} + T_{OFF}$$

$$T_{OFF} = 0.5 \text{ ms}$$

$$T_{ON} = 0.693 (R_A + R_B) C = 0.5 \text{ ms} \quad \text{Let } C = 0.1 \mu\text{F}$$

$$T_{OFF} = 0.693 (R_B) C = 0.5 \text{ ms}$$


$$R_A = \frac{0.5 \times 10^{-3}}{0.693 \times 0.1 \times 10^{-6}} = 7.2 \text{ k}\Omega$$

$$R_B = 7.2 \text{ k}\Omega$$



Design a Astable MV using 555 timer without using diode for foll spec

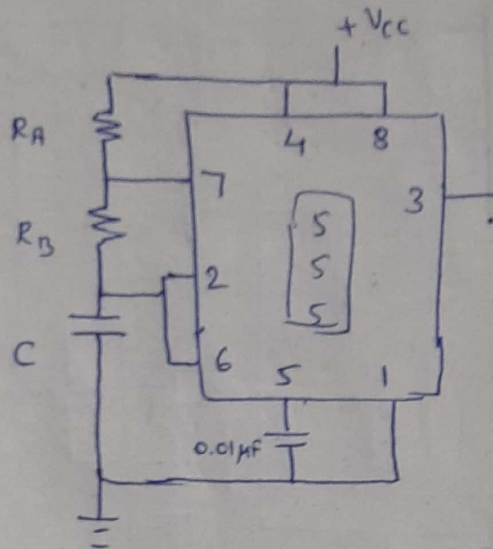① $f_{out} = 1 \text{ KHz}$, Duty cycle = 70%



$$T = \frac{1}{f} = 1 \text{ ms}$$

$$\text{Duty cycle} = \frac{T_{ON}}{T} = 0.7$$

$$T_{ON} = 0.7 \text{ ms}$$

$$T = T_{off} + T_{ON} = 1 \text{ ms}$$

$$C = 0.1 \mu \text{F}$$

$$T_{off} = 0.3 \text{ ms}$$

$$T_{ON} = 0.693 (R_A + R_B) C = 0.7 \text{ ms} \quad \text{--- ①}$$



$$T_{off} = 0.693 R_B C = 0.3 \text{ ms}$$

$$R_B = \frac{0.3 \times 10^{-3}}{0.693 \times 0.1 \times 10^{-6}} = 4.329 \text{ k}\Omega$$

$$\text{①} \Rightarrow R_A + 4.33 \times 10^3 = \frac{0.7 \times 10^{-3}}{0.1 \times 10^{-6} \times 0.693}$$



$$R_A = 5.77 \text{ k}\Omega$$

Monostable Multivibrator

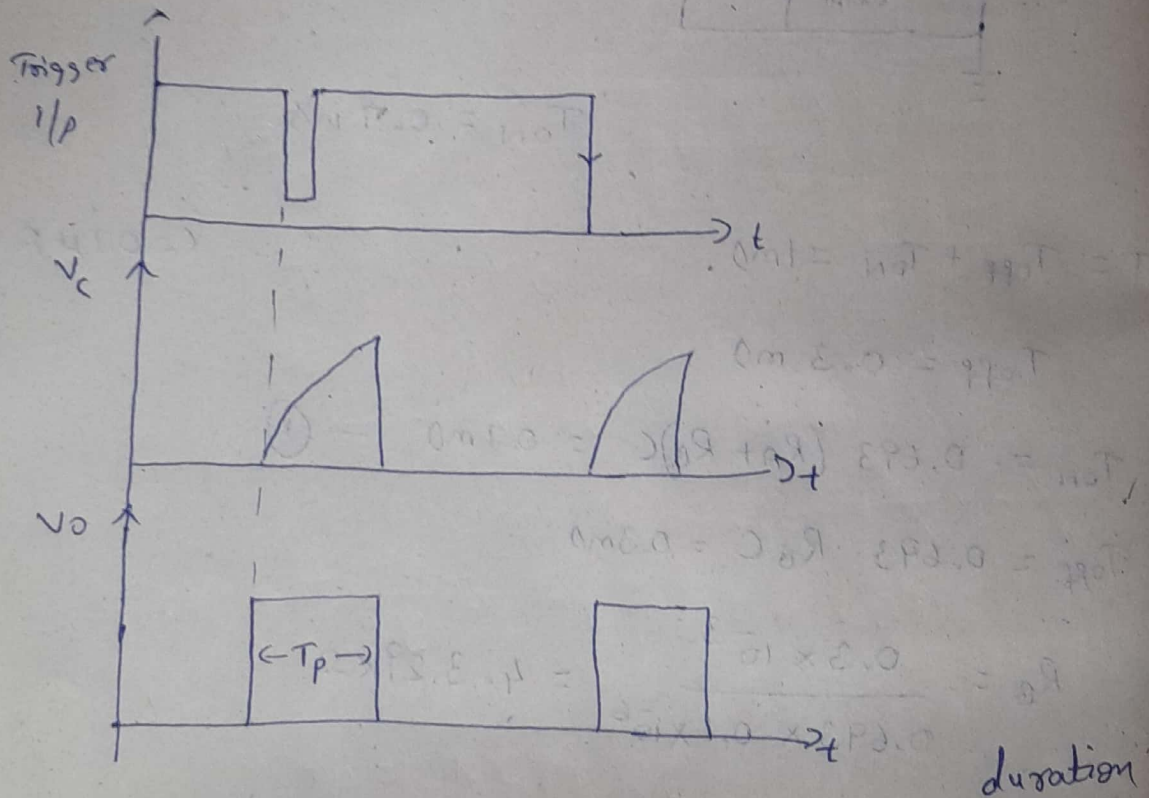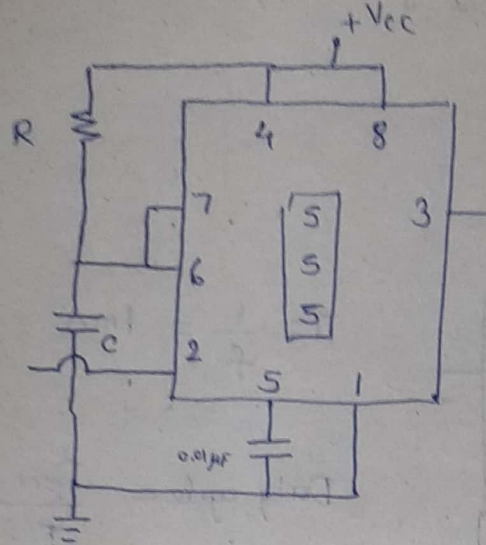

Appⁿ = Pulse stretching (If trigger \uparrow is longer)

	No change
R	0
S	0

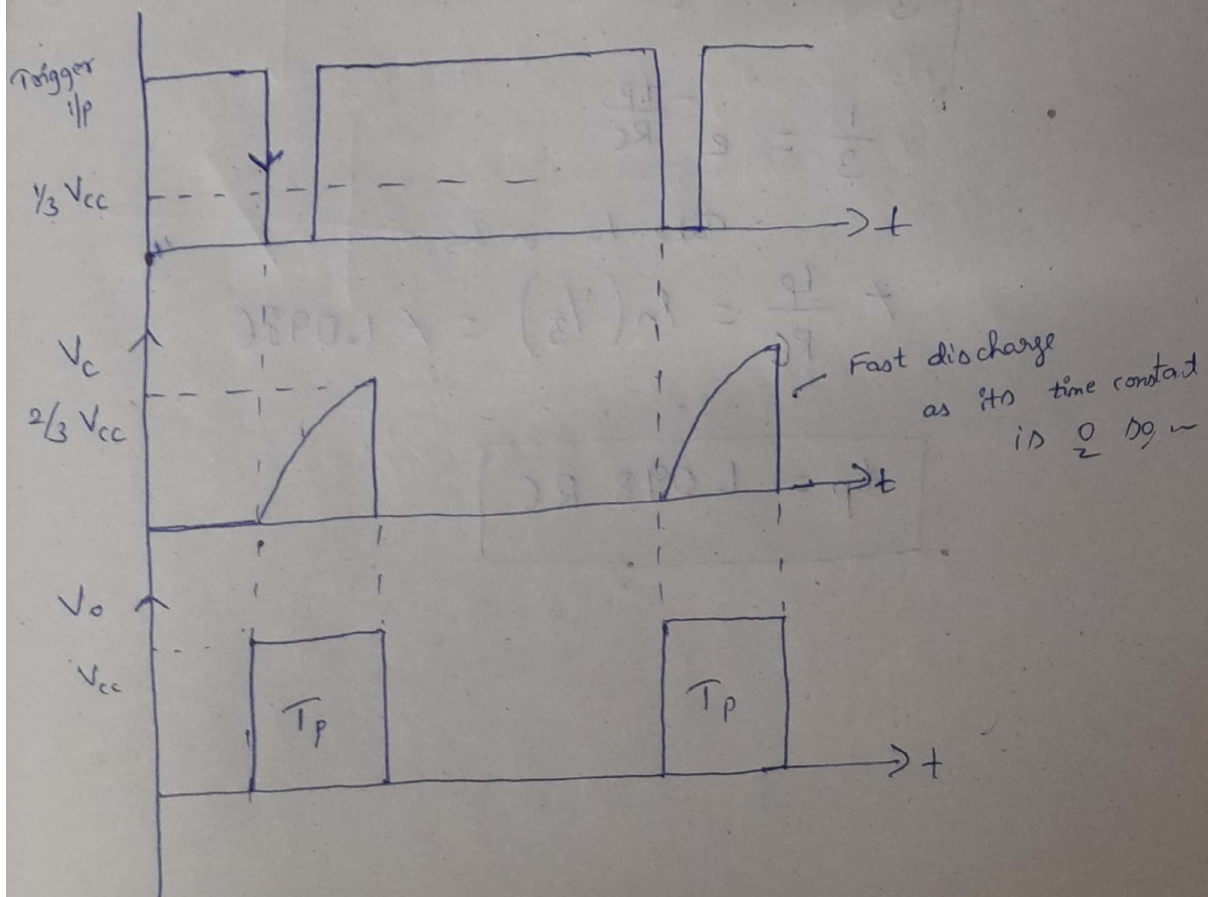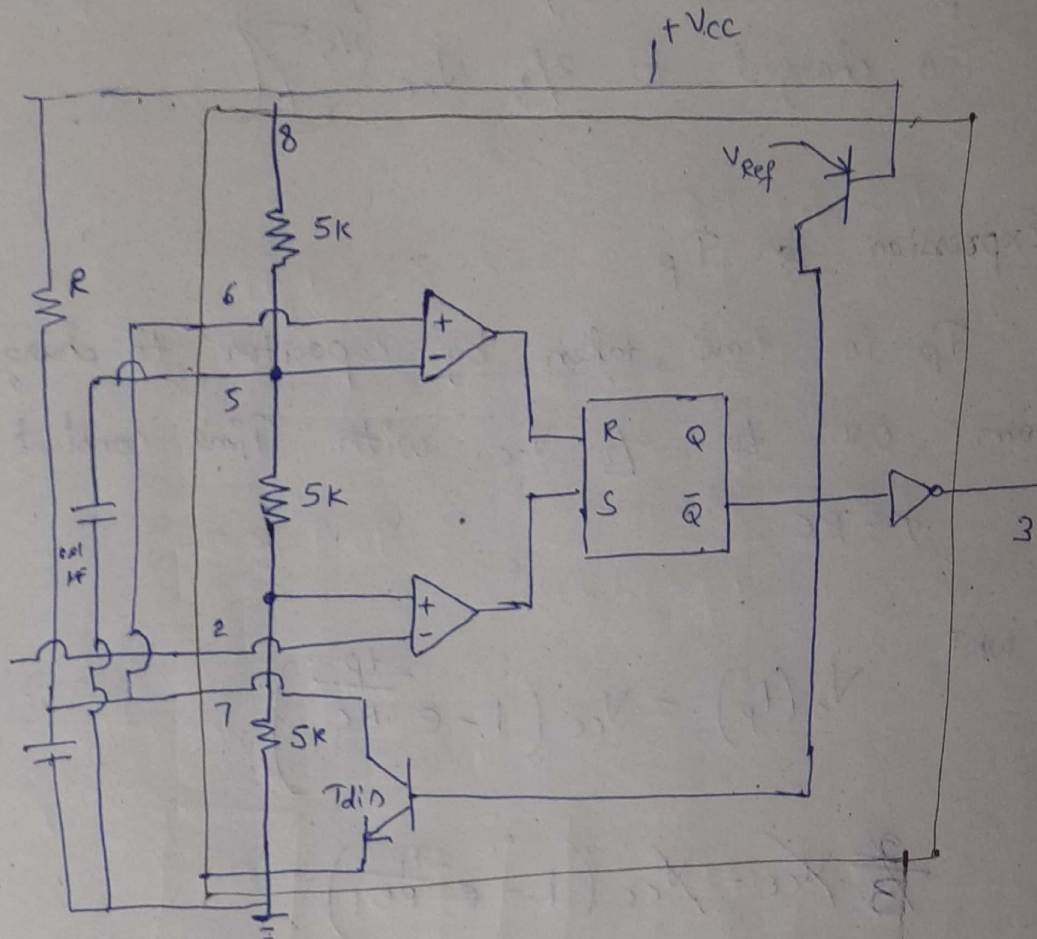

Applⁿ: Timer

→ T_p is decided by how fast the capacitor is charged to $\frac{2}{3} V_{cc}$

Expression for T_p

T_p is time taken by capacitor to charge from 0V to $\frac{2}{3} V_{cc}$ with time constant

$$\tau = RC$$

WKT

$$V_c(t_p) = V_{cc} \left(1 - e^{-\frac{t_p}{RC}} \right)$$

$$\frac{2}{3} V_{cc} = V_{cc} \left(1 - e^{-\frac{t_p}{RC}} \right)$$

$$\frac{2}{3} - 1 = -e^{-\frac{t_p}{RC}}$$

$$\frac{1}{3} = e^{-\frac{t_p}{RC}}$$



Take \ln on both sides

$$+\frac{t_p}{RC} = \ln\left(\frac{1}{3}\right) = -1.0986$$

$$t_p = 1.098 RC$$

→ For Trigger to happen $\Rightarrow T_{off} \ll t_p$

Monostable MV (without false triggering)

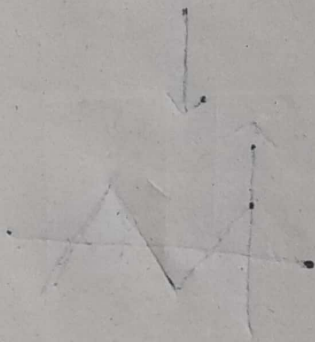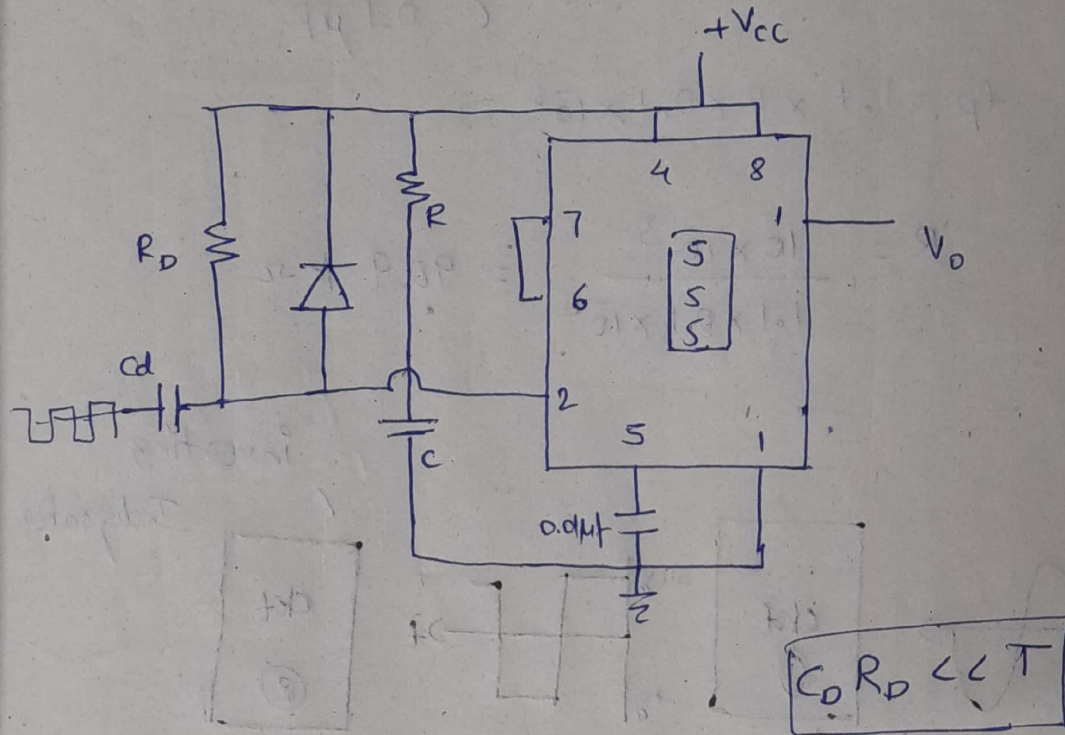


⑩ Design a Monostable MV which generate pulse
durⁿ 10 ms



$$t_p = 1.1 RC$$

$$C = 0.1 \mu F$$


$$t_p = 1.1 \times R \times 0.1 \times 10^{-6}$$
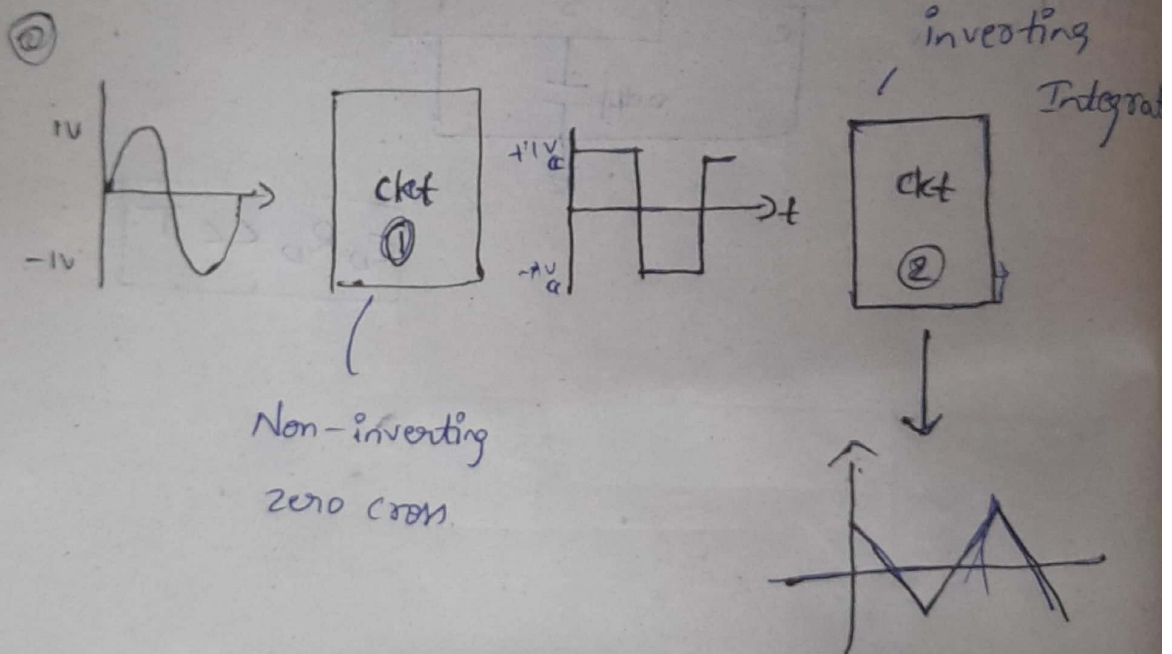
$$R = \frac{10 \times 10^{-3}}{1.1 \times 0.1 \times 10^{-6}} = 90.9 \text{ k}\Omega$$



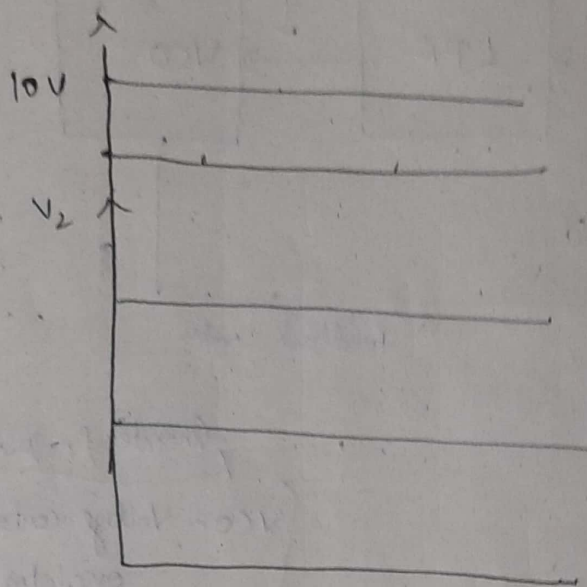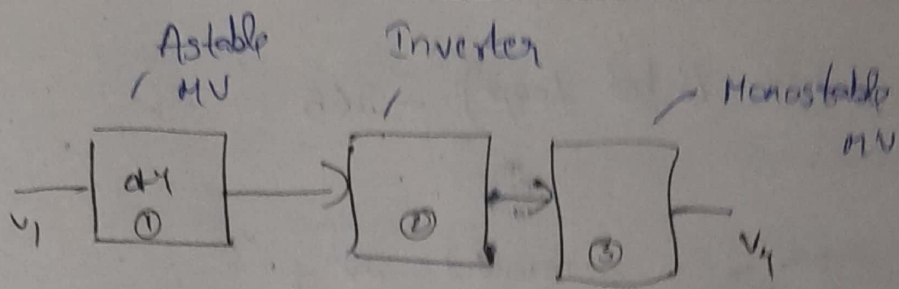

PLL (Phase Locked Loop) - 565

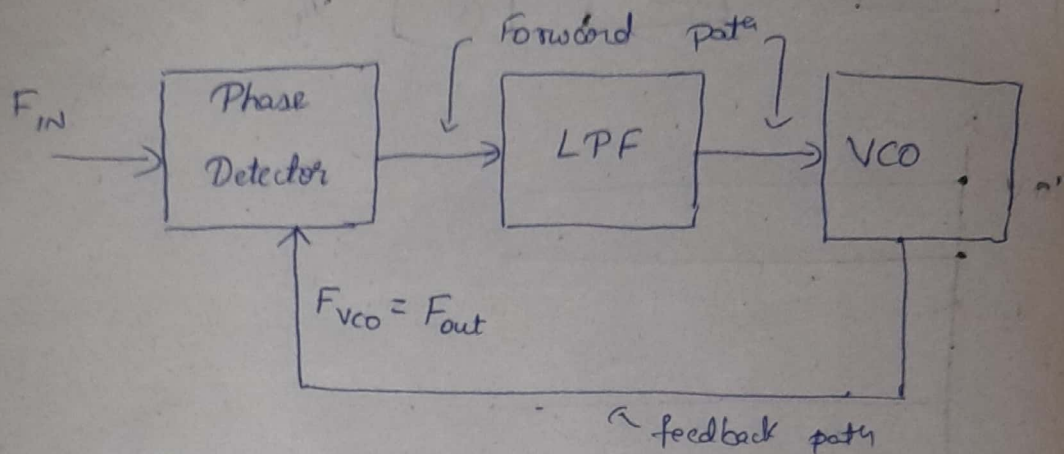


LPF \Rightarrow low pass filter,

Generate frequency
VCO - Voltage control oscillator
Loop freq depend on i/p volt

States

- * Free running
- * Capture
- * Lock

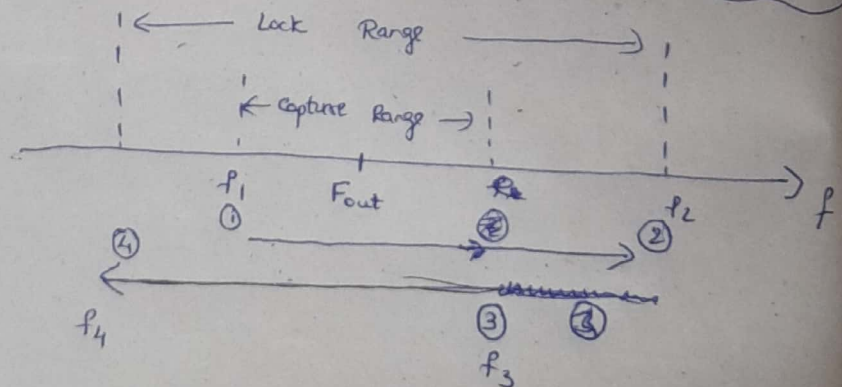

* Phase and frequency are dependent



* In capture range VCO freq is equal to i/p freq

Application

- ① Demodulation
- ② Frequency synthesis
- ③ Frequency division

- ④ FSK demodulation
(Frequency shift key)

Block diagram

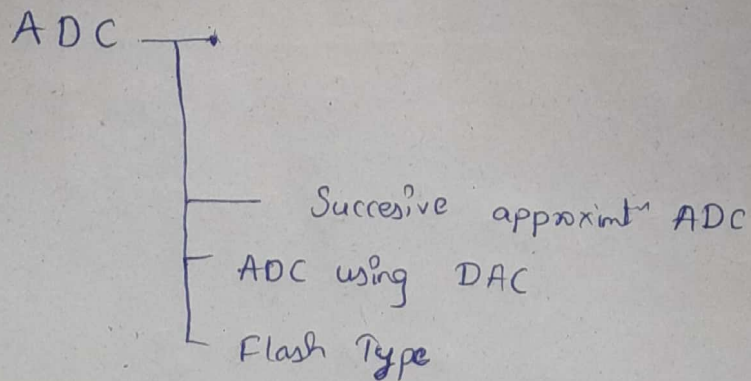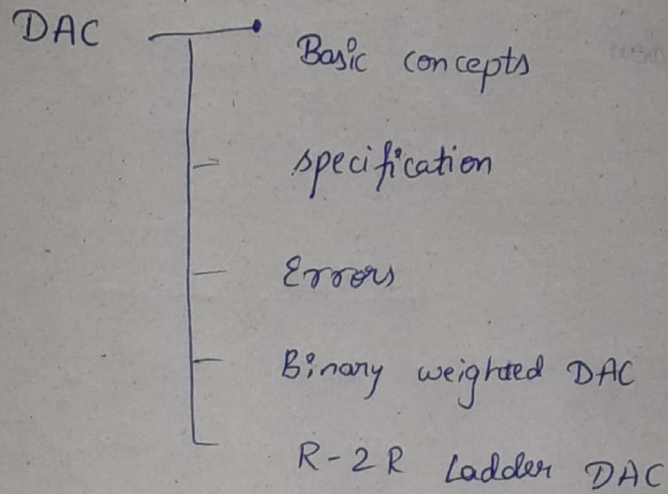


Analog: Continuous time cont signal & amplitude


ADC () Discrete time cont amplitude

DSP - Digital signal processing

Block diagram of A-D & D-A Conversion

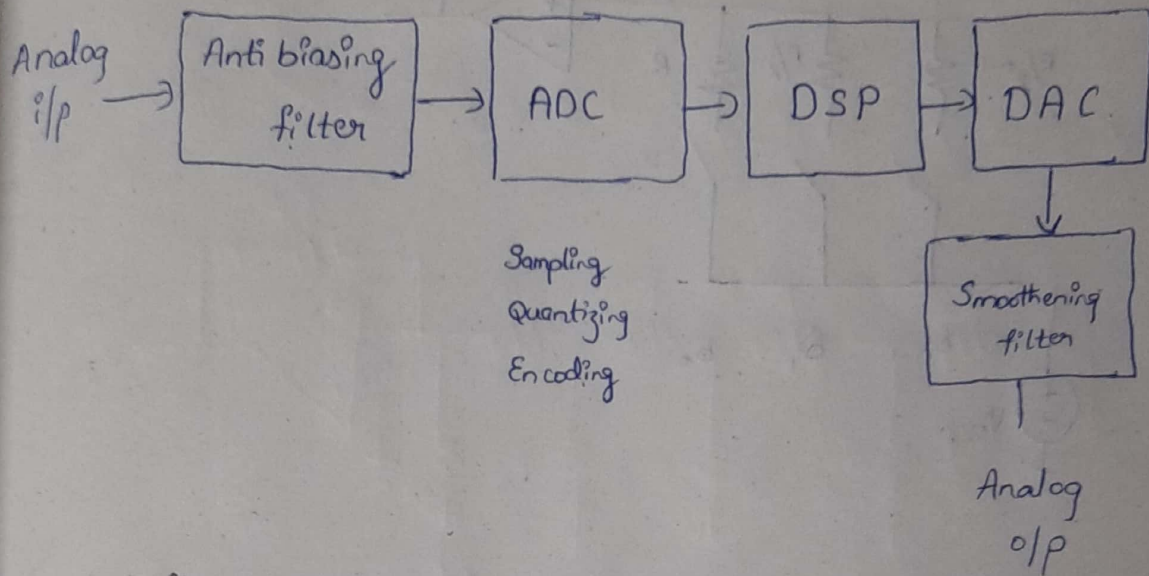


DAC

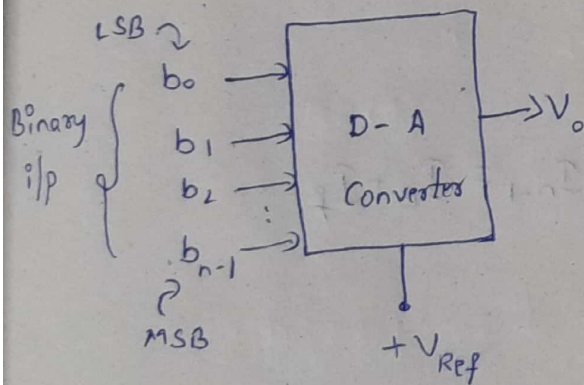


Binary weight

R-2R Ladder DAC

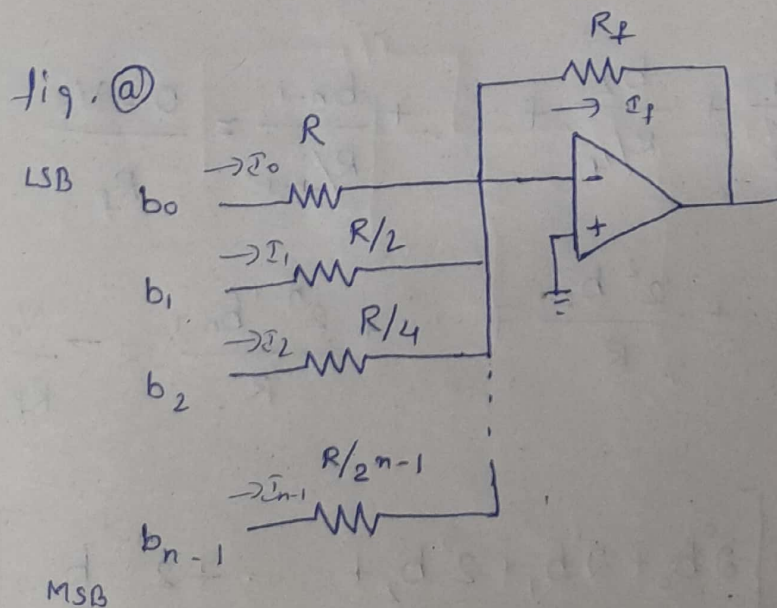

$$\frac{R}{2^n}$$

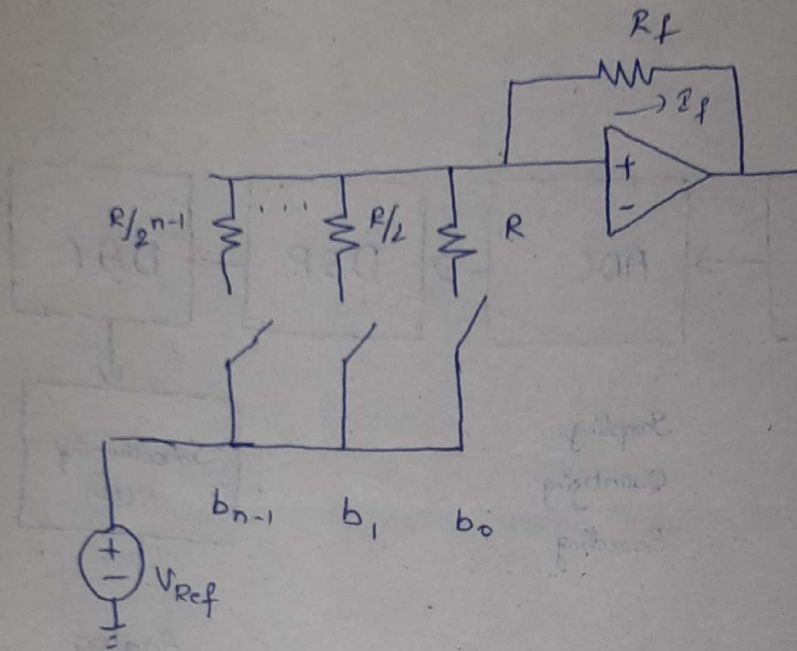

* LSB will have highest resistance

⇒ From fig (a)

$$I_0 + I_1 + I_2 + \dots + I_{n-1} = I_B + I_f$$

$$I_B = 0 \quad R_i = \infty$$

$$I_0 + I_1 + I_2 + \dots + I_{n-1} = I_f$$

$$\frac{b_0}{R} + \frac{b_1}{R/2} + \frac{b_2}{R/4} + \dots + \frac{b_{n-1}}{R/2^{n-1}} = \frac{0 - V_o}{R_f}$$

$$\frac{b_0}{R} + \frac{2b_1}{R} + \frac{2^2 b_2}{R} + \dots + \frac{2^{n-1} b_{n-1}}{R} = -\frac{V_o}{R_f}$$

$$V_o = -\frac{R_f}{R} \left[2^0 b_0 + 2^1 b_1 + 2^2 b_2 + \dots + 2^{n-1} b_{n-1} \right]$$

Here $b_i = 0$


$b_i = +V_{ref}$ for binary data '1'

* So for b_i is high it is V_{ref}

$$V_o = - \frac{R_f}{R} \times V_{ref} \left[b_0 + 2^1 b_1 + 2^2 b_2 + \dots + 2^n b_{n-1} \right]$$

for b_i should be '1' or '0'

⇒

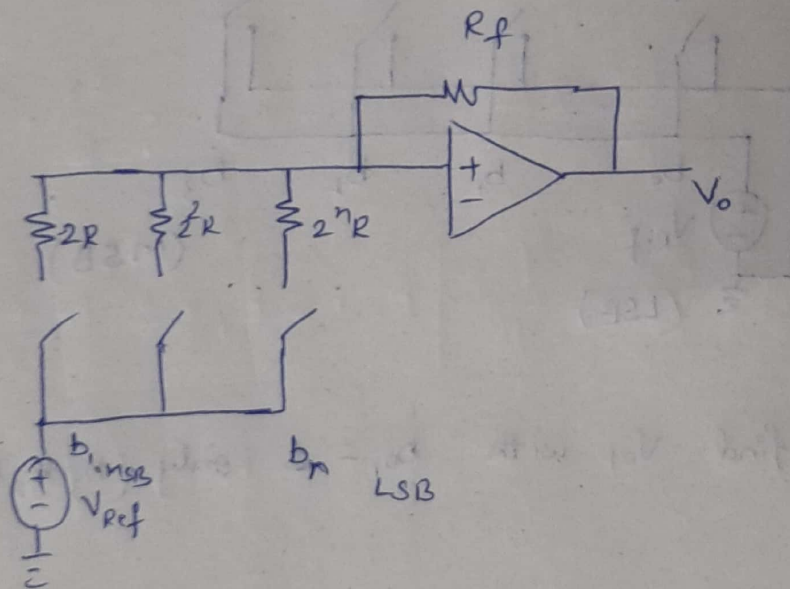

$$V_o = - \frac{R_f}{R} \times V_{ref} \left[\frac{b_1}{2^1} + \frac{b_2}{2^2} + \dots + \frac{b_n}{2^n} \right]$$

MSB LSB


Advantage

Easy to Design


Disadvantage

Availability of standard weighted resistance is difficult

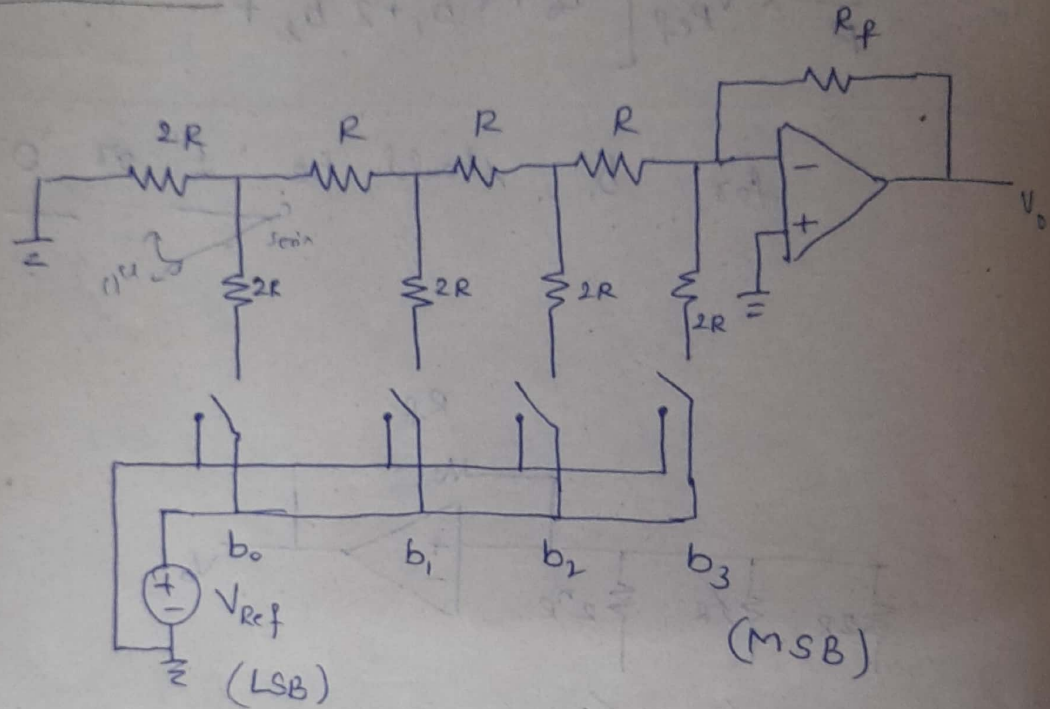Lab R-2R ckt / Advantage: Requires only 2 type Res







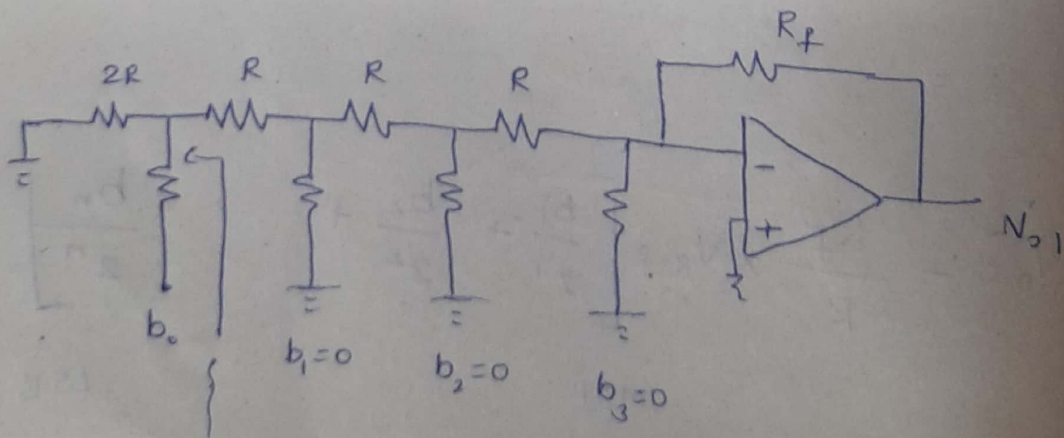To find V_{o1} with $b_0 = 1$ only ($b_3 b_2 b_1 b_0 = 0001$)



Apply thevenin eqn

Using thevenin's eqⁿ

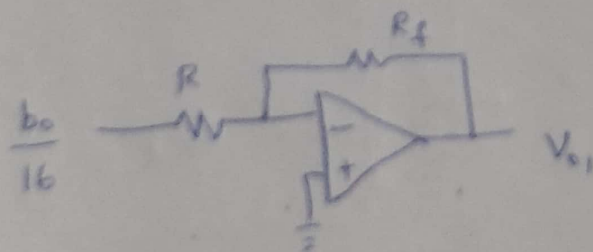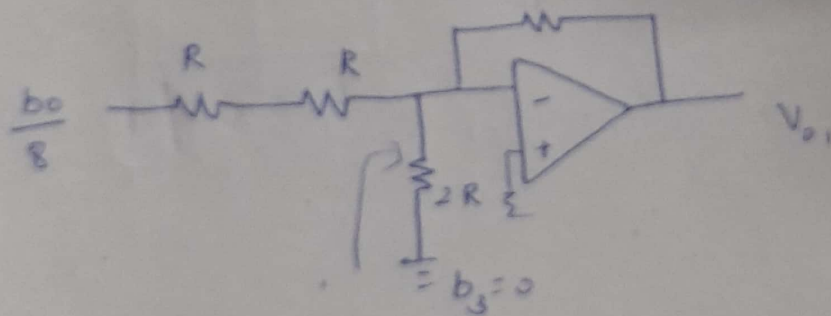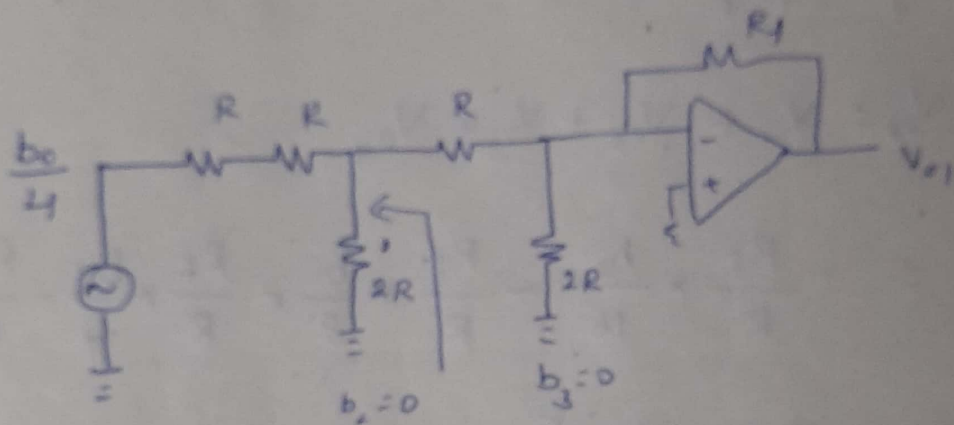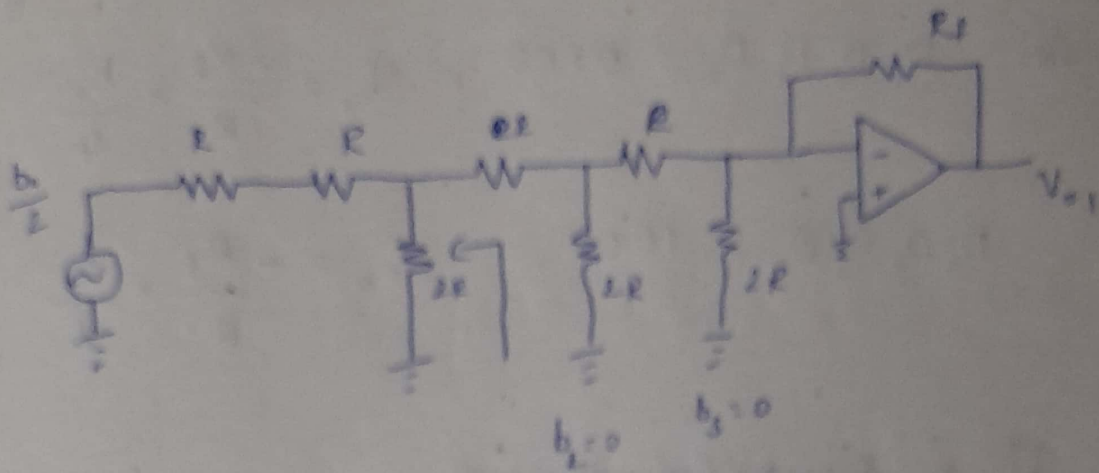

$$V_{o1} = - \frac{R_f}{R} \times \frac{b_0}{16}$$

11⁴ for $D_3 D_2 D_1 D_0 = 0010$, $V_{02} = -\frac{R_f}{R} \times \frac{b_1}{8}$

for $D_3 D_2 D_1 D_0 = 0100$, $V_{03} = -\frac{R_f}{R} \times \frac{b_2}{4}$

$D_3 D_2 D_1 D_0 = 1000$, $V_{04} = -\frac{R_f}{R} \times \frac{b_3}{2}$

Using superposition theorem

$$V_{0s} = V_{01} + V_{02} + V_{03} + V_{04}$$

$$= -\frac{R_f}{R} \times \frac{b_0}{16} - \frac{R_f}{R} \times \frac{b_1}{8} - \frac{R_f}{R} \times \frac{b_2}{4} - \frac{R_f}{R} \times \frac{b_3}{2}$$

$$V_o = -\frac{R_f}{R} \times \frac{V_{Ref}}{16} \left[b_0 + 2b_1 + 2^2 b_2 + 2^3 b_3 \right]$$

$$b_i = 0 / 1$$